

100/100

Tristan Denning


## ECE 310 – Microelectronics I

Dr. Suat Ay


**Homework #7**  
Due Date: 11/29/2021

Fall 2021

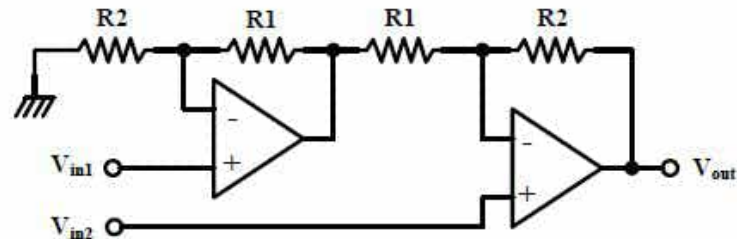
1. **(10 points)** Find the input-output relation ( $V_{out}$  versus  $V_{in1}$  and  $V_{in2}$ ), using ideal Opamp model.



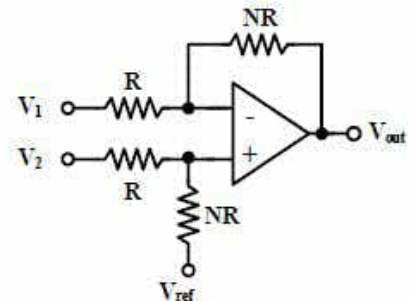
2. **(20 points)** Find the input-output relation ( $V_{out}$  versus  $N$ ,  $V_{ref}$ ,  $V_1$  and  $V_2$ ) using non-ideal Opamp model and verify that your derivation is correct. (NR means;  $N$  times  $R$ )



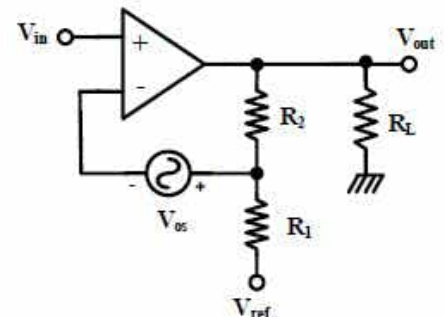3. **(30 points)** Find the input-output relation ( $V_{out}$  versus  $V_{in}$ ,  $V_{os}$  and  $V_{ref}$ ) under following conditions.  
a. Find it using ideal Opamp model.  
b. Verify that your derivation is correct.



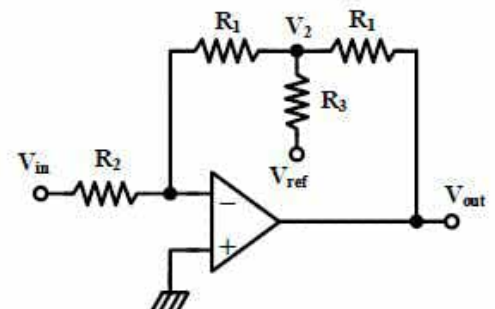
4. **(40 points)** For the circuit shown, assume  $R_1=100K$ ,  $R_2=10K$ , and  $R_3=1K-100K$  (a potentiometer/trimmer).  
a. The input-output relation and voltage gain expression of the circuit using ideal OPAMP model.  
b. Verify that your derivation is correct.  
c. Calculate the voltage gain for minimum and maximum values of the  $R_3$  (for  $V_{ref}=0$ ).  
d. Derive the voltage gain expression using non-ideal OPAMP model and verify that your derivation is correct for  $V_{ref}=0$ .



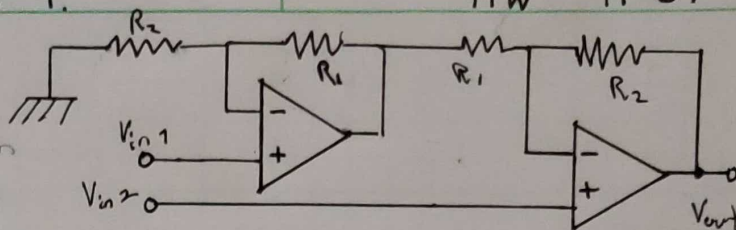1.


Situation:

Find the input-output relation ( $V_{out}$  vs  $V_{in1}$  and  $V_{in2}$ ), using the ideal op-amp model.



2 Goal: To determine the i/o relationship between  $V_{out}$  and the two inputs,  $V_{in1}$  and  $V_{in2}$ .

3 Plan: To utilize the "3-zero" Rule and ideal opamp characteristics along with the fundamental circuit analysis techniques to determine a relation for the output in terms of the input.

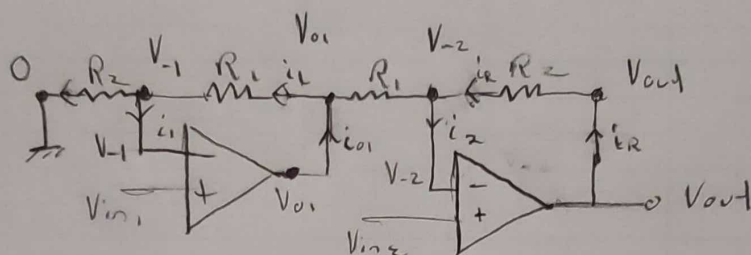4 Solution:Redraw:Observe:

$$\begin{aligned} i_1 &= i_2 = 0 \\ V_{in1} &= V_{+1} = V_{-1} \\ V_{in2} &= V_{+2} = V_{-2} \end{aligned}$$

KCL  $V_{-1}$ 

$$\frac{(V_{o1} - V_{-1})}{R_1} = \frac{V_{-1}}{R_2}$$

$$\therefore V_{o1} = \frac{V_{-1}(R_1)}{R_2} + V_{-1}$$

$$\therefore V_{o1} = V_{in1} \left( 1 + \frac{R_1}{R_2} \right)$$

KCL  $V_{-2}$ 

$$\frac{(V_{out} - V_{-2})}{R_2} = \frac{(V_{-2} - V_{o1})}{R_1}$$

$$(V_{out} - V_{-2})R_1 = (V_{-2} - V_{o1})R_2$$

$$V_{out}R_1 = V_{-2}R_1 + V_{-2}R_2 - V_{o1}R_2$$

$$V_{out} = V_{in2} + \frac{V_{in2}R_2}{R_1} - V_{in1} \left( 1 + \frac{R_1}{R_2} \right) \frac{R_2}{R_1}$$

$$= V_{in2} \left( 1 + \frac{R_2}{R_1} \right) - V_{in1} \left( 1 + \frac{R_2}{R_1} \right)$$

$$\therefore \boxed{V_{out} = (V_{in2} - V_{in1}) \left( 1 + \frac{R_2}{R_1} \right)}$$

7

 (continued)Sanity Check

Unit analysis:

$$V_{out} = (V_{in2} - V_{in1}) \left( 1 + \frac{R_2}{R_1} \right)$$

$$[V] = ([V] - [V]) \left( 1 + \frac{[\Omega]}{[\Omega]} \right)$$

$$= [V] ([-])$$


$$= [V] \checkmark$$

Units check out and process was straightforward.



2

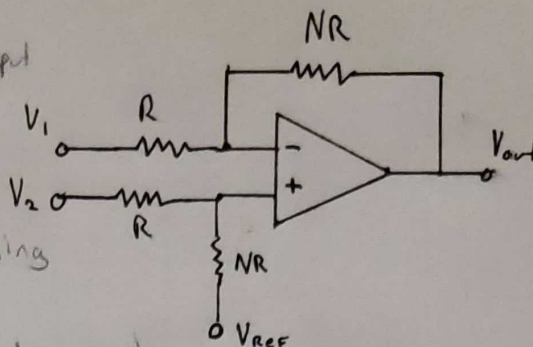1 Situation: Find The input-output relation ( $V_{out}$  vs  $N$ ,  $V_{ref}$ ,  $V_1$  and  $V_2$ ) using Non-ideal opamp model and Verify the derivation.




2 Goal: To determine an expression relating  $V_{out}$  to  $V_1$ ,  $V_2$ ,  $V_{ref}$ , and  $N$ .

3 Plan: To Utilize the "2-zero" rule and nonideal opamp characteristics along with the fundamental circuit analysis techniques to determine a relation for the output in terms of  $V_1$ ,  $V_2$ ,  $V_{ref}$ , and  $N$ .

4 Solution:

Redraw/Label:

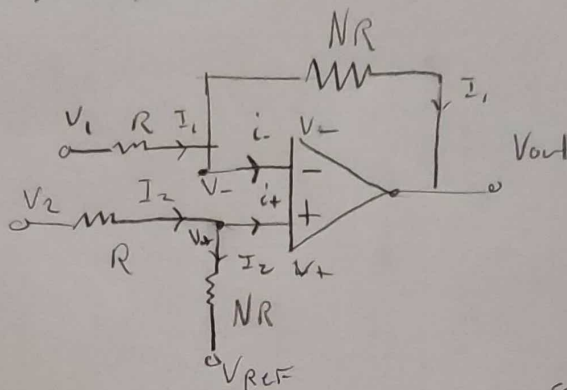

Observe:

$$I_+ = I_- = 0$$

$\therefore$  "2-zero"

$$V_{out} = A_o (V_+ - V_-)$$

(1)

KCL  $V_-$

$$\frac{(V_1 - V_-)}{R} = \frac{(V_- - V_{out})}{NR}$$

$$(V_1 - V_-) = \frac{(V_- - V_{out})}{N}$$

$$V_1 - V_- = V_- + \frac{V_-}{N} - \frac{V_{out}}{N}$$

$$V_1 + \frac{V_{out}}{N} = V_- \left(1 + \frac{1}{N}\right)$$

$$\therefore V_- = \frac{\left(V_1 + \frac{V_{out}}{N}\right)}{\frac{N+1}{N}}$$

$$V_- = \frac{NV_1 + V_{out}}{N+1}$$

(2)

2 (Continued)

$$\text{KCL } V_+ \quad \frac{(V_2 - V_+)}{R} = \frac{V_+ - V_{REF}}{NR}$$

$$\therefore V_+ = \frac{NV_2 + V_{REF}}{N+1} \quad (3)$$

$$(2), (3) \rightarrow (1): V_{out} = A_o \frac{1}{N+1} \left( (NV_2 + V_{REF}) - (NV_1 + V_{out}) \right)$$

$$V_{out} = A_o \frac{1}{N+1} (NV_2 + V_{REF}) - \frac{A_o V_1 N}{N+1} - \frac{A_o V_{out}}{N+1}$$

$$V_{out} \left( 1 + \frac{A_o}{N+1} \right) = \frac{A_o}{N+1} (NV_2 + V_{REF} - NV_1)$$

$$\therefore V_{out} = \frac{\frac{A_o}{N+1} (NV_2 + V_{REF} - NV_1)}{\left( 1 + \frac{A_o}{N+1} \right)}$$

$$= \frac{A_o (NV_2 + V_{REF} - NV_1)}{(N+1 + A_o)}$$

$$\therefore \boxed{V_{out} = \frac{A_o (NV_2 + V_{REF} - NV_1)}{N+1 + A_o}}$$

Verify: Use Ideal Model, then check  $\lim_{A_o \rightarrow \infty} (V_{out})$   
For Non-Ideal

$$V_+ = V_-$$

$$\therefore NV_2 + V_{REF} = NV_1 + V_{out}$$

$$\therefore V_{out, ideal} = NV_2 + V_{REF} - NV_1$$

2

 (Continued)Sanity Check:

$$\text{Check } \lim_{A_o \rightarrow \infty} (V_{out}) \stackrel{?}{=} V_{out, Ideal}$$

$$\lim_{A_o \rightarrow \infty} \left( \frac{A_o (NV_2 + V_{REF} - NV_1)}{N+1 + A_o} \right)$$

$$= \frac{\infty (NV_2 + V_{REF} - NV_1)}{\infty + (N+1)}$$

$$= \frac{\infty (NV_2 + V_{REF} - NV_1)}{\infty}$$

$$= NV_2 + V_{REF} - NV_1$$

$$= V_{out, Ideal}$$

$$\therefore \lim_{A_o \rightarrow \infty} (V_{out}) = V_{out, Ideal}$$


So the derivation for  $V_{out}$  using Non-Ideal opAmp model is correct

$$\text{Simplified: } V_{out} = \frac{A_o(N(V_2 - V_1) + V_{REF})}{A_o + N + 1}$$



3

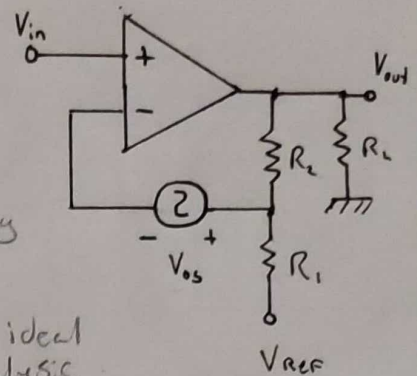Situation: Find the input-output relation ( $V_{out}$  vs  $V_{in}$ ,  $V_{os}$ , and  $V_{ref}$ ) for the given circuit. a.) Use ideal opamp model b.) Verify the derivation is correct.




Goal: To relate  $V_{out}$  to  $V_{in}$ ,  $V_{os}$ ,  $V_{ref}$  using ideal opamp model, then verify.

Plan: To use the "3-zero" rule along with ideal opamp characteristics and fundamental circuit analysis techniques - including Superposition - to determine the relation and then verify the derivation.

Solution:

Redraw/Label

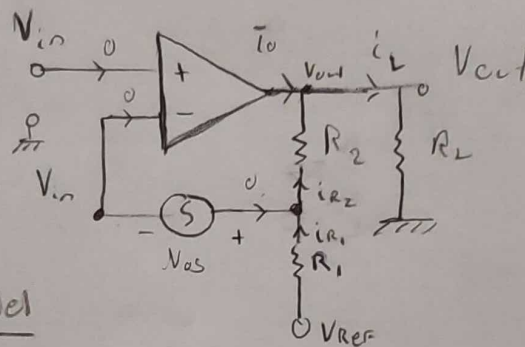

a.) Ideal Opamp Model

Observe:  $i_{R2} = i_{R1}$

$$V_{R1} = V_{in} + V_{os}$$

"3-Zero Rule"

$$KCL + V_{os}: \frac{(V_{in} + V_{os}) - V_{out}}{R_2} = \frac{V_{ref} - (V_{in} + V_{os})}{R_1}$$

$$((V_{in} + V_{os}) - V_{out}) R_1 = (V_{ref} - (V_{in} + V_{os})) R_2$$


$$V_{in} R_1 + V_{os} R_1 - V_{out} R_1 = V_{ref} R_2 - V_{in} R_2 - V_{os} R_2$$

$$R_1(V_{in} + V_{os}) - R_2(V_{ref} - V_{in} - V_{os}) = V_{out} R_1$$

$$V_{out} = (V_{in} + V_{os}) - (V_{ref} - (V_{in} + V_{os})) \frac{R_2}{R_1}$$

$$V_{out} = (V_{in} + V_{os}) - (V_{ref} - (V_{in} + V_{os})) \frac{R_2}{R_1} \quad (1)$$

3

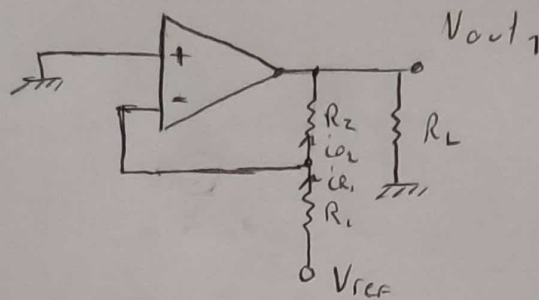 (continued)
b.) Verify derivation from a.)Superposition 1.) Set  $V_{in} = 0$ ,  $V_{os} = 0$ ,  $V_{ref} \neq 0$ RedrawObserve:

$$V_+ = V_- = -V_{os} = 0 \quad \therefore \text{Grounded}$$


$$\therefore V_{os} = 0$$

then

$$i_{R1} = i_{R2}$$

$$\frac{V_{ref} - 0}{R_i} = \frac{-V_{out1}}{R_2}$$

$$V_{out1} = -V_{ref} \frac{R_2}{R_i} \quad (*)$$

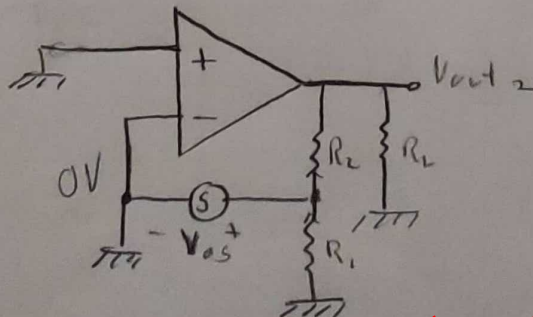Superposition 2.) Set  $V_{ref} = 0$ ,  $V_{in} = 0$ ,  $V_{os} \neq 0$ Redraw:Observe:

$$V_{in} = V_+ = V_- = -V_{os}$$

$$i_{R1} = i_{R2}$$




3 (continued)

$$\frac{0 - V_{os}}{R_1} = \frac{V_{os} - V_{out2}}{R_2}$$

$$-V_{os} \frac{R_2}{R_1} - V_{os} = -V_{out2}$$

$$V_{os} \left(1 + \frac{R_2}{R_1}\right) = V_{out2} \quad (*)$$

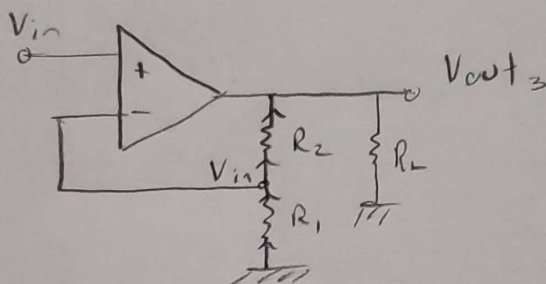Superposition 3:  $V_{in} \neq 0$ ,  $V_{os} = 0$ ,  $V_{ref} = 0$



$$\frac{0 - V_{in}}{R_1} = \frac{V_{in} - V_{out3}}{R_2}$$

$$\therefore V_{out3} = V_{in} \left(1 + \frac{R_2}{R_1}\right) \quad (*)$$

Add  $V_{out1} + V_{out2} + V_{out3}$ , Check  $= V_{out}$

$$\Rightarrow -V_{REF} \frac{R_2}{R_1} + V_{os} \left(1 + \frac{R_2}{R_1}\right) + V_{in} \left(1 + \frac{R_2}{R_1}\right)$$

$$= -V_{REF} \frac{R_2}{R_1} + V_{os} + V_{os} \frac{R_2}{R_1} + V_{in} + V_{in} \frac{R_2}{R_1}$$

$$= (V_{os} + V_{in}) + \frac{R_2}{R_1} (-V_{REF} + V_{os} + V_{in})$$

$$= (V_{os} + V_{in}) - (V_{REF} - (V_{os} + V_{in})) \frac{R_2}{R_1}$$

$$= \textcircled{1}$$

3

(continued)

5 Sanity Check:

Topology Check: The given looks like it is Almost a Non-inverting Amp. Set  $V_{as}, V_{ref} = 0$  to check

$$V_{out} = (V_{in} + V_{as}) - (V_{ref} - (V_{in} + V_{as})) \frac{R_2}{R_1}$$

$$V_{out} |_{V_{as}=V_{ref}=0} = V_{in} - (0 - (V_{in})) \frac{R_2}{R_1}$$

$$= V_{in} + V_{in} \frac{R_2}{R_1}$$

$$= \left(1 + \frac{R_2}{R_1}\right) V_{in} \quad \checkmark$$

For a non-inverting Amp,  $V_{out} = \checkmark V_{in} \left(1 + \frac{R_2}{R_1}\right)$

Since I verified my expression for  $V_{out}$  in part a.) with Superposition in b.), and the topology Check worked, I am Confident in my expression


# Tristan Denning Problem 4 (a.)

HW #07

**4(a.) Situation:** For the circuit

shown, assume  $R_1 = 100k$ ,  $R_2 = 10k$ ,  $R_3 = 1k - 100k$ .

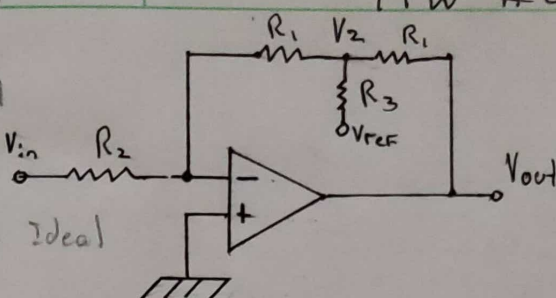a.) Find the i/o relation and voltage gain expression using the ideal opamp model.




**Goal:** To determine an expression relating  $V_{out}$  to  $V_{in}$ ,  $V_{ref}$ ,  $V_2$  and the resistors, then find  $A_v = V_{out}/V_{in}$  for the given amplifier.

**Plan:** To use the fundamental circuit analysis techniques along with the "3-zero" rule to derive a relationship between  $V_{out}$  and the inputs.

**4 Solution:**

Redraw/Label:

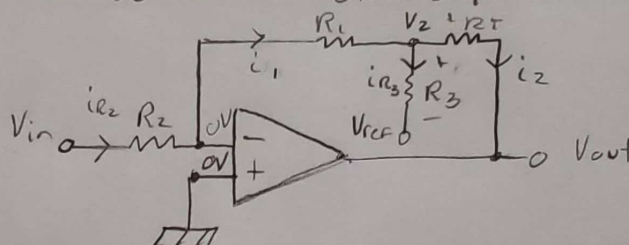

Observe:

$$V_+ = V_- = 0$$

$$i_{R2} = i_1$$

$\therefore$  "3-zero" rule

KCL  $V_-$

$$\frac{V_{in} - 0}{R_2} = \frac{0 - V_2}{R_1}$$

$$\frac{V_{in}}{R_2} = -\frac{V_2}{R_1}$$

$$\therefore V_2 = -V_{in} \frac{R_1}{R_2} \quad (1)$$

KCL  $V_2$

$$i_1 = i_{R3} + i_2$$

$$\frac{0 - V_2}{R_1} = \frac{V_2 - V_{ref}}{R_3} + \frac{V_2 - V_{out}}{R_1}$$

$$-V_2 \left( \frac{1}{R_1} \right) = V_2 \left( \frac{1}{R_3} \right) - V_{ref} \left( \frac{1}{R_3} \right) + V_2 \left( \frac{1}{R_1} \right) - V_{out} \left( \frac{1}{R_1} \right)$$

$$V_{out} \left( \frac{1}{R_1} \right) = V_2 \left( \frac{1}{R_1} + \frac{1}{R_1} + \frac{1}{R_3} \right) - V_{ref} \left( \frac{1}{R_3} \right)$$

$$V_{out} = V_2 \left( 2 + \frac{R_1}{R_3} \right) - V_{ref} \cdot \frac{R_1}{R_3} \quad (2)$$



**4(a)** (continued)

$$\textcircled{1} \rightarrow \textcircled{2} \quad V_{out} = -V_{in} \frac{R_1}{R_2} \left( 2 + \frac{R_1}{R_3} \right) - V_{ref} \cdot \frac{R_1}{R_3}$$

$$V_{out} = -V_{in} \frac{100k}{10k} \left( 2 + \frac{100k}{R_3} \right) - V_{ref} \left( \frac{100k}{R_3} \right)$$

$$V_{out} = -V_{in} \left( 10 \left( 2 + \frac{100k}{R_3} \right) \right) - V_{ref} \left( \frac{100k}{R_3} \right)$$

$$V_{out} = -V_{in} \left( 20 + \frac{1000k}{R_3} \right) - V_{ref} \left( \frac{100k}{R_3} \right)$$

For  $V_{ref} = 0$

$$V_{out} = -V_{in} \left( 20 + \frac{1000k}{R_3} \right)$$


$$\therefore \frac{V_{out}}{V_{in}} = - \left( 20 + \frac{1000k}{R_3} \right) \quad \checkmark$$

$$A_v = - \left( 20 + \frac{1000k}{R_3} \right) \quad \checkmark$$

Sanity Check:

See Part 4(b).

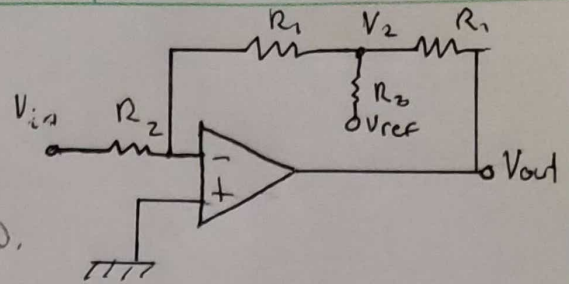**4(b)** 1 Situation: For the gain expression determined in 4(a), Verifying that it is correct



2 Goal: To Verify the result for 4(a).


3 Plan: To use a topology check to Verify the gain expression determined in 4(a).

4 Solution:

Sanity Check For 4(a):

Impose Inverting amplifier by setting  $V_{ref} = 0$ ,  $R_3 \rightarrow \infty$

Redraw

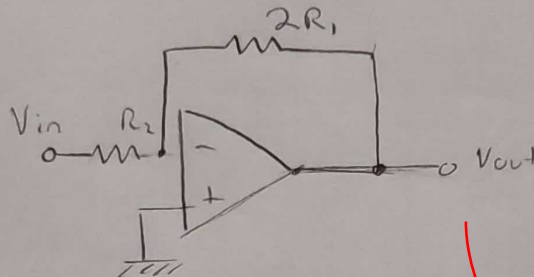

For inverting Amplifier (Ideal):

$$A_{v,inv} = -\frac{2R_1}{R_2} = -\frac{200k}{10k}$$

$$A_{v,inv} = -20$$

Impose  $V_{ref} = 0$ ,  $R_3 \rightarrow \infty$  to  $A_v$  From 4(a).

$$A_v = -\left(20 + \frac{1000k}{R_3}\right)$$

$$\lim_{R_3 \rightarrow \infty} (A_v) = -\left(20 + \frac{1000k}{\infty}\right)$$


$$= -20 + 0$$

$$= -20 \quad \checkmark$$

5 Sanity Check:

Imposing an inverting amplifier topology yields the same gain both mathematically, and by observation for known inverting Amp  $A_v$  equation

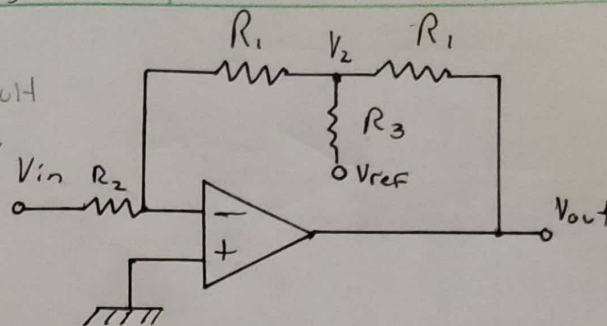**4(c)**, Situation: For the circuit shown with values given in 4(a), c.) Calculate the voltage gain for minimum and maximum values of  $R_3$  (let  $V_{ref} = 0$ ).



2Goal: To determine the circuit's gain at  $R_3 = 1k$ , and for  $R_3 = 100k$ .

3Plan: To evaluate the gain expression found in 4(a) for  $A_v|_{R_3=1k}$  and  $A_v|_{R_3=100k}$ .

4 Solution:

$R_3$  Minimum

$$A_v|_{R_3=1k} = -\left(20 + \frac{1000k}{1k}\right)$$

$$= \boxed{-1020 \left[\frac{V}{V}\right]}$$

$R_3$  Maximum

$$A_v|_{R_3=100k} = -\left(20 + \frac{1000k}{100k}\right)$$

$$= \boxed{-30 \left[\frac{V}{V}\right]}$$

$\therefore$  Assumption:  $V_{ref} = 0$


5Sanity Check:

This result makes sense.  $R_3$  acts as a controller for the inverting amplifier by increasing or decreasing the effective resistance between the  $V_-$  node and  $V_{out}$ .



4(d)

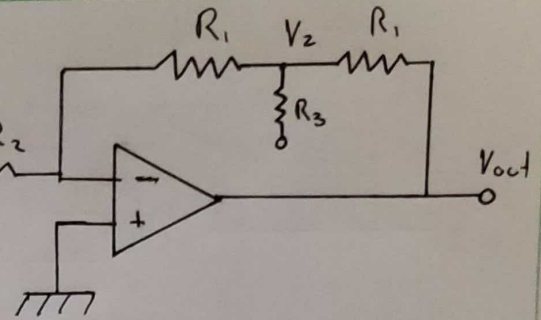
1 Situation: For the circuit shown, d.) Derive the voltage gain expression using non-ideal opamp model and verify correctness for  $V_{REF} = 0$ .



2 Goal: To derive an expression for the voltage gain using NON-ideal model.

Plan: To utilize "2-zero" rule along with NON-ideal opamp characteristics to derive an expression for the gain,  $A_v$  of the circuit.

Solution: Redraw:

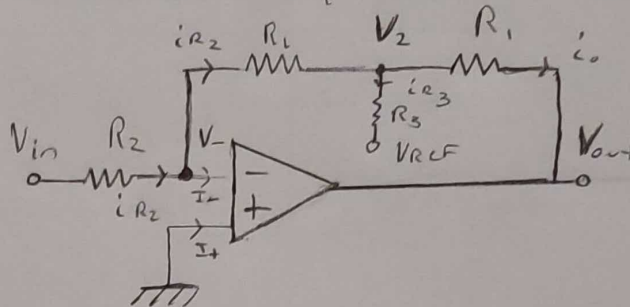

Observe:

$$I_+ = 0$$

$$I_- = 0$$

$$V_{out} = A_o(V_+ - V_-)$$

$$V_+ = 0 \Rightarrow V_{out} = -A_o V_- \quad (1)$$

KCL  $V_-$

$$i_{R2} = i_{R1}$$

$$\frac{V_{in} - V_-}{R_2} = \frac{V_- - V_2}{R_1}$$

$$(V_{in} - V_-)R_1 = (V_- - V_2)R_2$$

$$V_{in}R_1 + V_2R_2 = V_-(R_1 + R_2)$$

$$\therefore V_- = \frac{(V_{in}R_1 + V_2R_2)}{(R_1 + R_2)} \quad (2)$$

KCL  $V_2$

$$i_{R2} = i_o + i_{R3}$$

$$\frac{(V_- - V_2)}{R_1} = \frac{V_2 - V_{REF}}{R_3} + \frac{V_2 - V_{out}}{R_1}$$

$$\therefore V_2 = \frac{V_-R_3 + V_{REF}R_1 + V_{out}R_3}{R_1 + 2R_3} \quad (3)$$

$\therefore$  From Calculator

**4(d)** (Continued)

③ → ②

$$V_- = \frac{\left( V_{in} R_1 + \frac{(V_- R_3 + V_{ref} R_1 + V_{out} R_3) R_2}{(R_1 + 2R_3)} \right)}{R_1 + R_2} \quad (4)$$

④ → ①

$$V_{out} = -A_o \left( \frac{\left( V_{in} R_1 + \frac{(V_- R_3 + V_{ref} R_1 + V_{out} R_3) R_2}{R_1 + 2R_3} \right)}{R_1 + R_2} \right)$$

$$\frac{V_{out}}{V_{in}} = A_v = \frac{-20(R_3 + 50000) A_o}{100000 A_o V_{ref} + R_3(A_o + 21) + 1100000}$$

∴  $R_1 = 100k$ ,  $R_2 = 10k$ , Plugged into calculator to obtain  $A_v$  expression

$$\text{Now } A_v|_{V_{ref}=0} = \frac{-20(R_3 + 50000) A_o}{R_3(A_o + 21) + 1100000}$$

$$\therefore A_v = \frac{-20 A_o (R_3 + 50000)}{R_3(A_o + 21) + 1100000}$$

Sanity Check: Verifies  $V_{ref} = 0$  gain expression

$$\begin{aligned} \lim_{A_o \rightarrow \infty} (A_v) &= \frac{-20(\infty)(R_3 + 50000)}{R_3(\infty + 21) + 1100000} \\ &= \frac{-20(R_3 + 50000)}{R_3} \quad \therefore \text{Calculator} \\ &= -20 + \frac{1,000,000}{R_3} \quad \checkmark \end{aligned}$$

This is the same result as 4(a.)