

ECE 310 – Microelectronics I


Dr. Suat Ay

Homework #8
Due Date: 12/08/2021


Fall 2021

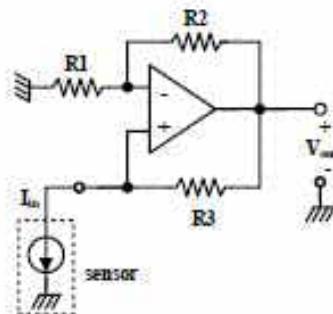1. (25pts) An OPAMP based sensor readout circuit is to be analyzed.

- (10 pts) Find transresistance gain ($A_R = V_{out}/I_{in}$) of the circuit using ideal OPAMP model.
- (10 pts) Find transresistance gain ($A_R = V_{out}/I_{in}$) of the circuit using non-ideal OPAMP model. Verify that your derivation is correct using part (a).
- (5 pts) Find input impedance of the circuit (R_{in}) that the sensor sees using non-ideal OPAMP model.




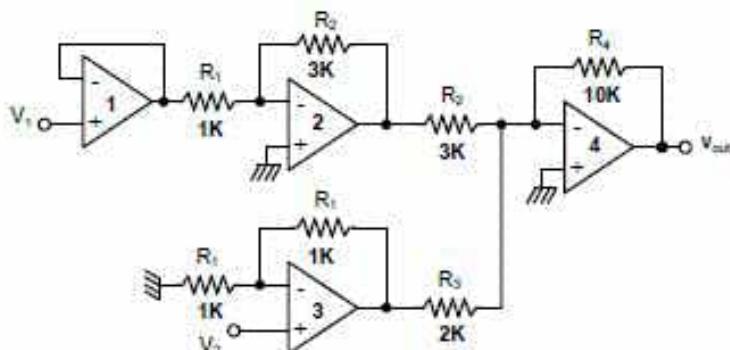2. (10 pts) Find V_{out} versus V_1 and V_2 . Use ideal OPAMP model for the circuit shown below.




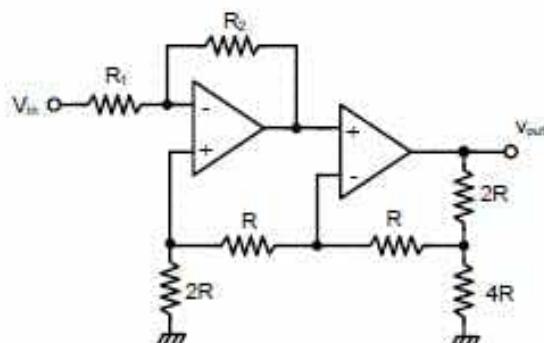3. (25points) Use ideal Opamp model for the circuit.


- (10 pts) Find V_{out} versus V_{in} expression
- (10pts) Verify that your derivation is correct using two different ways (unit check is not allowed).
- (5pts) Calculate transresistance gain if $R_1=2R_2$.



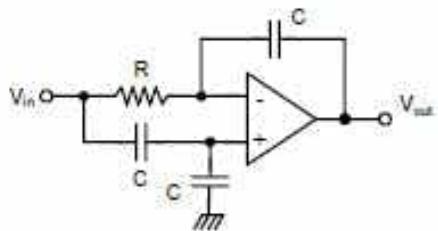
4. (10 pts) Find V_{out} versus V_{in} in time-domain. Use ideal OPAMP model.



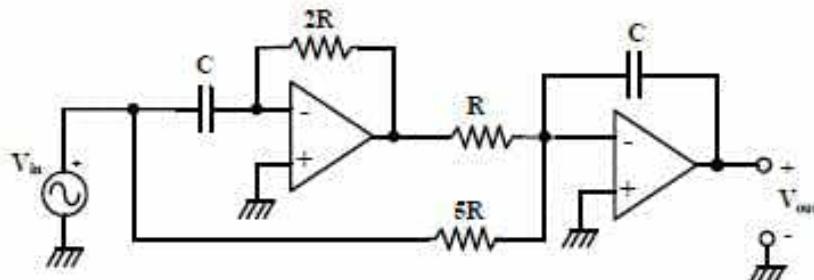
5. (10pts) Find the input-output relation of following circuit in time (t) domain (V_{out} versus V_{in}) using ideal OPAMP model.



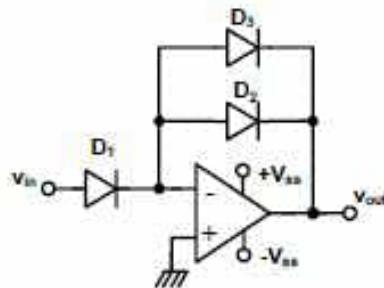6. (10 pts) Find the input-output relation of the following circuit. Use ideal OPAMP model, and assume all diodes are identical.



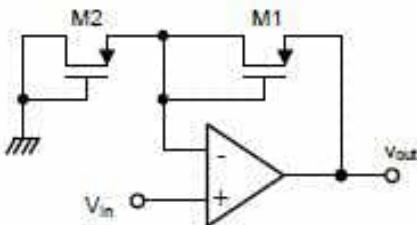7. (10 pts) Find input output relation V_{out} versus V_{in} . Use ideal Opamp model and $\lambda=0$ for MOSFET in the circuit shown below.



8. (10 points) Design an OPAMP based circuit that divides two inputs. Derive your circuit's input output relation (i.e. $V_{out}=A(V_{in1}/V_{in2})+B$) using ideal OPAMP model.

1(a.)

Situation: An opamp based Sensor feedback circuit is to be analyzed. a.) Find the transresistance gain $A_R = V_{out}/I_{in}$ of the circuit using Ideal Opamp Model


Goal: To use the "3-Zero" rule along with nodal analysis to derive an expression for $A_R = V_{out}/I_{in}$.

Plan: To use the "3-Zero" rule along with Nodal Analysis to derive an expression for the transresistance gain $A_R = V_{out}/I_{in}$.

Solution: Redraw/Label :

Observe:
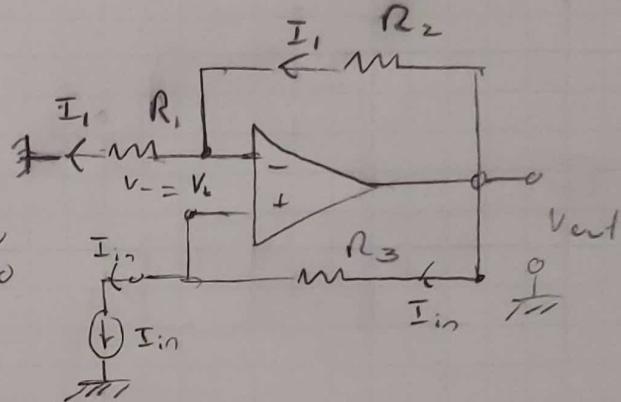
$$I_{R_1} = I_{R_2} = I_1 \quad \therefore I_2 = 0 \\ I_{in} = I_{R_3} \quad \therefore I_+ = 0 \\ V_+ = V_-$$



Nodal Analysis:

$$@ V_+ : \frac{(V_{out} - V_+)}{R_3} = I_{in}$$

$$\therefore V_+ = V_{out} - I_{in}R_3 = V_- \quad (1)$$

$$@ V_- : \frac{(V_{out} - V_-)}{R_2} = \frac{V_+}{R_1}$$

$$(V_{out} - V_-)R_1 = V_+R_2$$

$$V_{out}R_1 = V_+R_2 + V_-R_1$$

$$V_{out} = V_+ \left(\frac{R_2 + R_1}{R_1} \right)$$

$$(1) \Rightarrow V_{out} = (V_{out} - I_{in}R_3) \left(1 + \frac{R_2}{R_1} \right)$$

$$\therefore V_{out} = \frac{I_{in}(R_1 + R_2)R_3}{R_2}$$


$$\therefore A_R = \frac{(R_1 + R_2)R_3}{R_2}$$

5 Sanity Check:

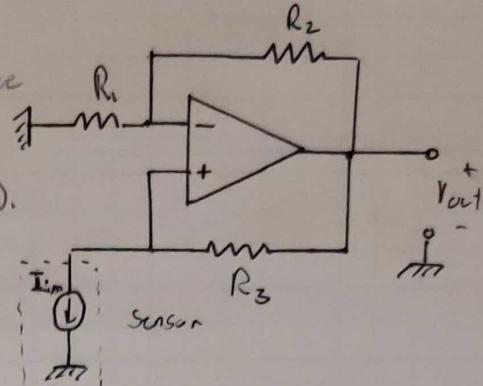Problem 1(b) will serve as Sanity check, Units check out.

1(b)

Situation: Find the transresistance gain ($A_R = \frac{V_{out}}{I_{in}}$) of the circuit using non-ideal opamp model. Verify the derivation is right from part 1(a).



Goal: Derive an expression for the Transresistance gain (A_R) using the Non-ideal opamp Model.

Plan: To use Nodal Analysis and the "2-zoo" rule and Non-ideal opamp Characteristics to derive an expression for A_R .


Solution: Redraw / Label

$$\text{Observe: } I_+ = I_- = 0$$

$$V_{out} = (V_+ - V_-)A_o$$

$$V_{out} = V_+ A_o - V_- A_o$$

$$V_+ = \frac{V_{out}}{A_o} + V_-$$

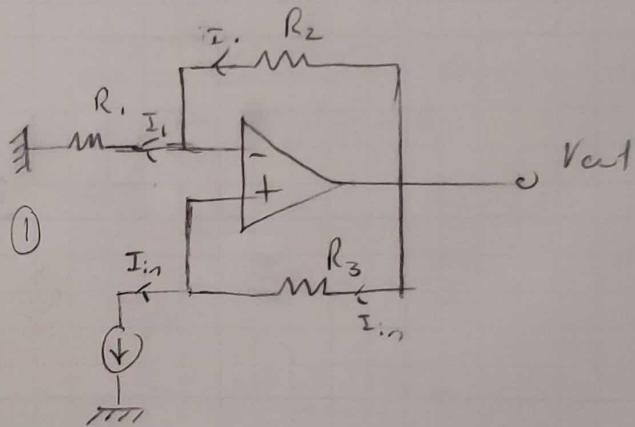

Nodal Analysis:

$$\textcircled{1} \quad V_- \quad \frac{(V_{out} - V_-)}{R_2} = \frac{V_-}{R_1}$$

$$(V_{out} - V_-)R_1 = V_- R_2$$

$$\therefore V_- = \frac{V_{out} \cdot R_1}{R_1 + R_2} \quad \textcircled{2}$$

$$\text{Nodal } \textcircled{2} \quad V_+ \quad \frac{(V_{out} - V_+)}{R_2} = I_{in}$$

$$\therefore V_+ = V_{out} - I_{in} R_3 \quad \textcircled{3}$$

$$\textcircled{3}, \textcircled{2} \Rightarrow \textcircled{1} \quad V_{out} = \left((V_{out} - I_{in} R_3) - \frac{V_{out} R_1}{R_1 + R_2} \right) A_o \quad \textcircled{4}$$

$$\text{Simplify 4: } V_{out} = \frac{-A_o I_{in} (R_1 + R_2) \cdot R_3}{R_1 - (A_o - 1) \cdot R_2}$$

1(b) (continued)

$$\therefore \frac{V_{out}}{I_{in}} = \boxed{\frac{-A_o (R_1 + R_2) \cdot R_3}{R_1 - (A_o - 1) \cdot R_2} = A_R}$$

Sanity Check (a), (b):

$$\text{Check } \lim_{A_o \rightarrow \infty} (A_{R, \text{Nonideal}}) = A_{R, \text{Ideal}}$$

$$\begin{aligned} \lim_{A_o \rightarrow \infty} (A_{R, \text{Nonideal}}) &= \frac{-\infty (R_1 + R_2) \cdot R_3}{R_1 - \infty R_2 + R_2} \\ &= \frac{-\frac{\infty}{\infty} (R_1 + R_2) \cdot R_3}{\frac{R_1}{\infty} - \frac{\infty}{\infty} R_2 + \frac{R_2}{\infty}} \\ &= \frac{-1 (R_1 + R_2) \cdot R_3}{0 - R_2 + 0} \end{aligned}$$

$$\boxed{A_R = \frac{(R_1 + R_2) \cdot R_3}{R_2}}$$

1(c) Situations: Find the input impedance (R_{in}) seen by the sensor using Non-ideal OPamp Model

Goal: To determine an expression for the circuit's input impedance, R_{in} .

3 Plan: To use the equation for $R_{in} = V_{in}/I_{in}$ and previously determined relations for V_{in} and I_{in} to derive an expression for R_{in} .

4 Solution:

$$R_{in} = \frac{V_+}{I_{in}}$$

$$V_+ = V_{out} - I_{in} R_3$$

$$\begin{aligned} \therefore R_{in} &= \frac{V_{out}}{I_{in}} - R_3 \\ &= \left(\frac{-A_o I_{in} (R_1 + R_2) \cdot R_3}{R_1 - (A_o - 1) \cdot R_2} \right) - R_3 \end{aligned}$$

$$\therefore R_{in} = \frac{-A_o (R_1 + R_2) \cdot R_3}{R_1 - (A_o - 1) \cdot R_2} - R_3$$

$$R_{in} = R_3 \left(\frac{-A_o (R_1 + R_2)}{R_1 - (A_o - 1) \cdot R_2} - 1 \right)$$

5 Sanity Check: Unit Analysis:

$$\begin{aligned} [\Omega] &= [\Omega] \left(\frac{-[-]([A] + [A])}{[A] - ([-]) \cdot [A]} - [-] \right) \\ &= [\Omega] [-] \\ &\equiv [\Omega] \quad \checkmark \end{aligned}$$

2.


Situation: Find V_{out} vs V_1 and V_2 using the Ideal opamp model for the circuit shown below:

$$R_1 = 1k$$

$$R_2 = 3k$$

$$R_3 = 2k$$

$$R_4 = 10k$$

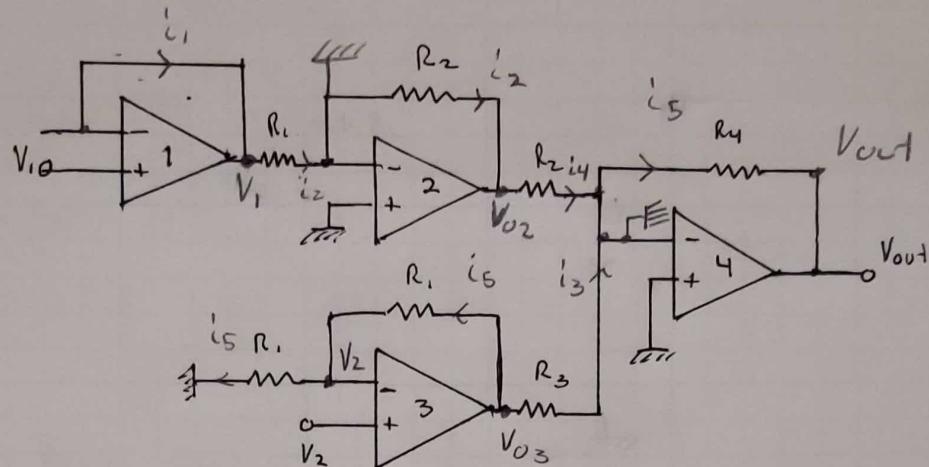

Goal: To derive an expression relating V_{out} to V_1 and V_2 .

Plan: To use the "3-zero" rule along with Nodal circuit analysis to develop a system of equations to solve for V_{out} in terms of V_1 , V_2 .

Solution: Label the given diagram:

Observations Under "3-zero" Rule:

$$V_1 = V_{+1} = V_{-1} = V_{out1}$$

$$V_{+2} = V_{-2} = 0$$

$$V_2 = V_{+3} = V_{-3}$$

$$V_{+4} = V_{-4} = 0$$

Nodal Analysis:

@ V_{-2} :

$$\frac{V_1}{R_1} = -\frac{V_{02}}{R_2}$$

$$\therefore V_{02} = -\frac{V_1 R_2}{R_1} \quad (1)$$

@ V_{-3} :

$$\frac{(V_{03} - V_2)}{R_1} = \frac{V_2}{R_1}$$

$$\therefore V_{03} = 2V_2$$

(2)

2 (continued)

$$\textcircled{2} \quad V_{-4}: i_4 + i_3 = i_5$$

$$\frac{V_{o2}}{R_2} + \frac{V_{o3}}{R_3} \doteq -\frac{V_{out}}{R_4} \quad \textcircled{3}$$

$$\textcircled{2}, \textcircled{1} \Rightarrow \textcircled{3}: \quad$$

$$-\frac{V_1}{R_1} + \frac{2V_2}{R_3} \doteq -\frac{V_{out}}{R_4}$$

$$V_{out} = R_4 \left(-\frac{V_1}{R_1} - \frac{2V_2}{R_3} \right)$$

$$R_4 = 10k, \quad R_1 = 1k, \quad R_3 = 2k$$

$$V_{out} = 10k \left(\frac{V_1}{1k} - \frac{2V_2}{2k} \right)$$

$$\boxed{V_{out} = 20(V_1 - V_2)}$$

Sanity Check:

This result makes sense because:

1) is a buffer with $V_{o1} = V_1$

2) is an inverting Amp with $V_{o2} = -V_{o1} \left(\frac{R_2}{R_1} \right)$

3) is a non-inverting Amp with $V_{o3} = V_2 \left(1 + \frac{R_1}{R_3} \right)$
 $= 2V_2$

then: 4) is a Summing Amplifier that adds the two, V_{o2}, V_{o3} and multiplies them by R_4/R_2 and R_4/R_3 respectively


The individual topologies combine to get the correct relation

3(a)

Situation: Find the V_{out} expression using Ideal model


Goal: To derive an expression relating V_{out} to V_{in} .

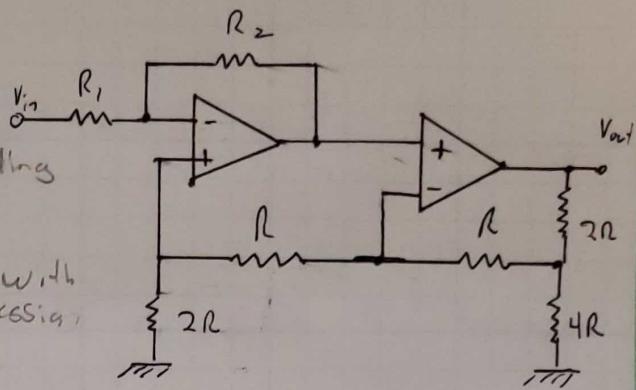Plan: To use "3-zero" Rule along with Nodal analysis to derive an expression relating V_{out} to V_{in} .



Solution: Redraw / Label.
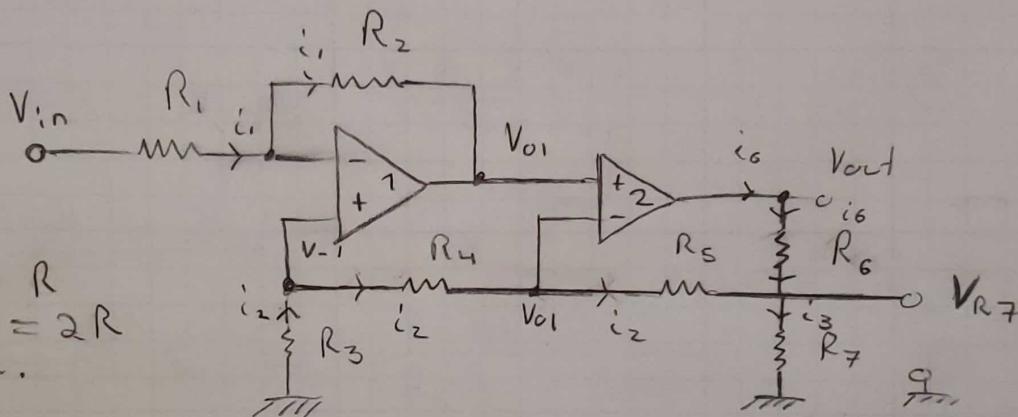
$$\begin{aligned} & \text{Let:} \\ & R_4 = R_5 = R \\ & R_3 = R_6 = 2R \\ & R_7 = 4R. \end{aligned}$$



Nodal @ V_{-1}

$$\frac{(V_{in} - V_{-1})}{R_1} = \frac{(V_{-1} - V_{o1})}{R_2} \quad (1)$$

@ V_{+1}

$$\frac{(-V_{-1})}{R_3} = \frac{(V_{-1} - V_{o1})}{R_4} \quad (2)$$

@ V_{-2}

$$\frac{(V_{-1} - V_{o1})}{R_4} = \frac{(V_{o1} - V_{R7})}{R_5} \quad (3)$$

@ V_{R7}

$$i_6 + i_2 = i_3$$

$$\frac{(V_{o1} - V_{R7})}{R_5} + \frac{(V_{out} - V_{R7})}{R_6} = \frac{V_{R7}}{R_7} \quad (4)$$

3(c) (continued)

* 4 eqn's, 4 unknowns W.R.T V_{out} : V_{in} , V_- , V_{o1} , V_{R7} .

∴ Solvable w/ Algebra

I will use my calculator to minimize the likelihood of error.

Solve ① For V_- :

$$\Rightarrow V_- = \frac{(V_{o1}R_1 + V_{in}R_2)}{R_1 + R_2} \quad ⑤$$

⑤ → ② For V_{o1} :

$$\Rightarrow V_{o1} = \frac{-V_{in}R_2(3R)}{R_1 \cdot R - 2R_2R} \quad ⑥$$

⑥, ⑤ → ③ For V_{R7} :

$$\Rightarrow V_{R7} = \frac{(V_{o1} - V_{in})R_2}{(R_1 + R_2)} + V_{o1} \quad ⑦$$

Solve ⑥, ⑦, and ④ For V_{out}

$$V_{out} = 2V_{R7} \quad ⑧$$

$$= 2 \left(\frac{\left[\frac{(-V_{in}R_2(3R))}{R_1 \cdot R - 2R_2R} - V_{in} \right] R_2}{R_1 + R_2} + \frac{(-V_{in}R_2(3R))}{R_1 \cdot R - 2R_2R} + V_{o1} \right)$$

$V_{out} =$	$\frac{-8V_{in}R_2}{R_1 - 2R_2}$
	$8/22$

Sanity Check

Part 3(b) is
Sanity Check

3(b)

Situation: Verify the derivation from 3(a), using two different methods. Unit Check is not allowed.

Goal: To verify the result from 3(a) using two methods.


Plan: To Δ to an inverting Amp

and Vice-Versa then solve the system's for V_{out} and compare to their mathematical equivalent operations to the expressions found in 3(a).

Solution:

1) $\Delta \Rightarrow$ inverting Amp, $\Delta \Rightarrow$ Non inverting;

Redraw:

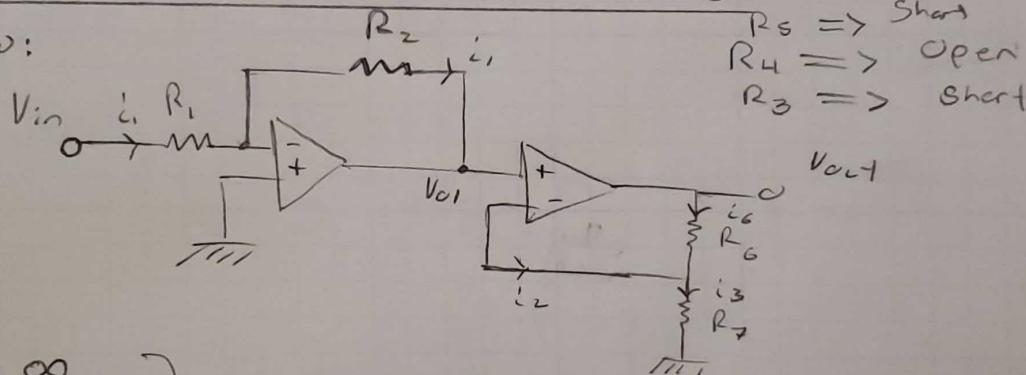

$$R_4 = \infty$$

$$R_3 = 0$$

$$V_- = 0$$

Expected V_{o1} :

$$V_{o1} = -\frac{R_2}{R_1} V_{in}$$

Check eqn ① from Part 3(a):

$$\frac{(V_{in} - V_-)}{R_1} = \frac{(V_- - V_{o1})}{R_2}$$

$$\frac{V_{in}}{R_1} = -\frac{V_{o1}}{R_2} \quad \therefore V_- = 0$$

$$\therefore V_{o1} = -\frac{R_2}{R_1} V_{in}$$

So eqn 1 holds true for $R_4 = \infty$, $R_3 = 0$.

3(b) (continued)

Check eqn ② From 3(a) For $R_4 = \infty$, $R_3 = 0$

$$\ast V_{-1} = 0$$

$$\therefore \frac{-V_{-1}}{R_3} = \frac{(V_{-1} - V_{o1})}{R_4}$$

$$0 = \frac{-V_{o1}}{\infty}$$

$$0 = 0$$

So eqn ② holds true for the conditions

Check eqn for V_{out} ⑧

$$V_{out} = 2 V_{R7}$$

$$= 2 \left(\frac{(V_{o1} - V_{in}) R_2}{R_1 + R_2} + V_{o1} \right)$$

$$= 2 \left(\frac{\left(\frac{-R_2}{R_1} V_{in} - V_{in} \right) \cdot R_2}{R_1 + R_2} + -\frac{R_2}{R_1} V_{in} \right)$$

$$= -\frac{4 R_2 V_{in}}{R_1} = -4 V_{in} \frac{R_2}{R_1}$$

For noninverting amp, the output

$$\text{should be } V_{out} = \left(1 + \frac{R_o}{R_7} \right) V_{o1}$$

$$V_{out} = \left(1 + \frac{2R}{4R} \right) \left(-\frac{R_2}{R_1} V_{in} \right)$$

$$= \dots$$

3(b) (continued)

s Sanity Check:

I'm not sure how to conveniently do a topology check, because any resistors that I could remove are a multiple of R . So if I short one, $R=0$, or open one, $R=\infty$, this changes the circuit parameters completely.

Furthermore, If I did solve the new V_{out} expressions, I will not be able to relate them to my original expression from 3(a).

So I will continue to Part c.) under the assumption my result from a.) is correct.

I did check it with multiple sets of equations.

$$V_{out} = \frac{-8V_{in}R_2}{R_1 - 2R_2}$$

3(c)

Situation: Calculate transresistance gain if $R_1 = 2R_2$.

Goal: To calculate the transresistance gain for $R_1 = 2R_2$.

Plan: To Set $R_1 = 2R_2$ then use the transresistance gain equation to solve for the transresistance gain. $A_R = V_{out}/I_{in}$

Solution:

$$\text{Equation: } A_R = \frac{V_{out}}{I_{in}}$$

$$V_{out} = \frac{-8V_{in}R_2}{R_1 - 2R_2}$$

$$\frac{V_{out}}{V_{in}} = A_v = \frac{-8R_2}{R_1 - 2R_2}$$

$$A_R = R_{in} \times A_v$$

$$R_{in} = R_1$$

∴ Lecture 37

$$\therefore A_R = \frac{-8R_1R_2}{R_1 - 2R_2}$$

Slide 4.

$$\text{For } R_1 = 2R_2$$

$$A_R = \frac{-8R_1R_2}{0} \rightarrow \infty$$


$$\therefore A_R \rightarrow \infty$$

Sanity Check: This can also be verified with:

$$A_R = \frac{V_{out}}{I_{in}} = \frac{\left(\frac{-8V_{in}R_2}{2R_1 - 2R_2}\right)}{I_{in}} = \frac{\infty}{I_{in}}$$

$$= \infty \quad \checkmark$$

$\boxed{12/22}$

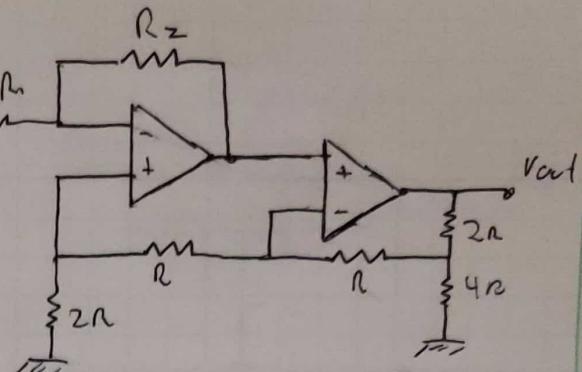

4

Situation: Find V_{out} vs V_{in} in the time domain for the given OpAmp. Use Ideal opamp model.

Goal: To derive the input-output relation for the given amplifier.


Plan: To use the "3-zero" rule and capacitor current equation along with Nodal analysis to derive a relation between V_{out} and V_{in} .

Solution: Redraw / Label

$$V_+ = V_- \\ I_+ = I_- = 0$$

$$V_{in} = 2V_C$$

$$V_+ = V_C = \frac{V_{in}}{2}$$

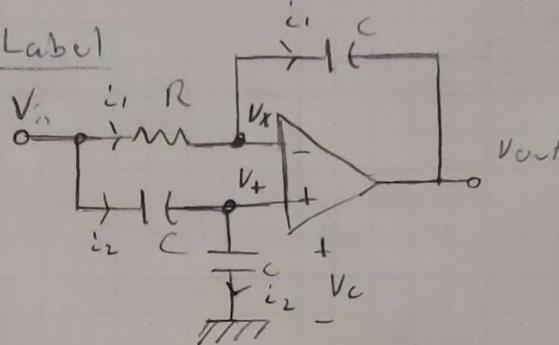

Nodal @ V_- :

$$\frac{(V_{in} - V_+)}{R} = C \frac{d(V_+ - V_{out})}{dt}$$

$$\therefore \frac{(V_{in} - \frac{V_{in}}{2})}{R} = C \frac{d(\frac{V_{in}}{2} - V_{out})}{dt}$$

$$V_{in} = 2RC \left(\frac{dV_{in}}{dt} \cdot \frac{1}{2} - \frac{dV_{out}}{dt} \right)$$

$$\frac{1}{2RC} (V_{in} dt) = \frac{dV_{in}}{2} - dV_{out}$$


$$\frac{1}{2RC} \int_{t_1}^{t_2} V_{in} dt = \frac{1}{2} \int dV_{in} - \int dV_{out}$$

$$\frac{1}{2RC} \int_{t_1}^{t_2} V_{in}(t) dt = \frac{V_{in}}{2} - V_{out}$$

$$\therefore \boxed{V_{out} = \frac{V_{in}}{2} - \frac{1}{2RC} \int_{t_1}^{t_2} V_{in}(t) dt}$$

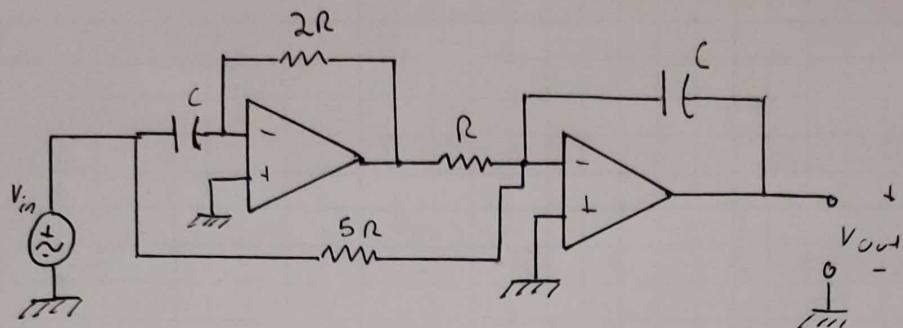5.


Situation: Find the input-output relation for the following circuit in the time domain, Using the Ideal opamp model:



Goal: To find the time domain relation of V_{out} to V_{in} under the ideal opamp model.

Plan: To use the "3-zero" rule, Nodal analysis, as well as the time domain capacitor current equation to derive an expression relating V_{out} to V_{in} .

Solution: Redraw / Label:

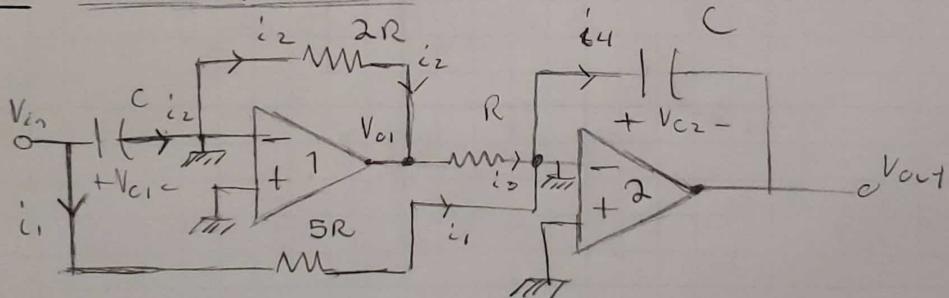

Observe:

$$V_{in} = V_{c1}$$

$$V_{out} = -V_{c2}$$

$$i_1 = \frac{V_{in}}{5R} = \frac{V_{c1}}{5R}$$

$$\text{Nodal @ } V_1 \text{ Node: } i_2 = C \frac{dV_{c1}(t)}{dt} = C \frac{dV_{in}(t)}{dt}$$

$$\therefore C \frac{dV_{in}(t)}{dt} = -\frac{V_{o1}}{2R}$$

$$\therefore V_{o1} = -2RC \frac{d}{dt}(V_{in}(t)) \quad (1)$$

5 (Continued)

Nodal @ V₂ Node: $i_1 + i_3 = i_4$

$$\frac{V_{o1}}{R} + \frac{V_{in}}{5R} = C \frac{dV_{o2}(t)}{dt}$$

$$\therefore \frac{V_{o1}}{R} + \frac{V_{in}}{5R} = -C \frac{d}{dt}(V_{out}(t))$$

$$5V_{o1} + V_{in} = -5RC \frac{d}{dt} V_{out}(t)$$

$$-\frac{V_{o1}}{RC} dt - \frac{V_{in}}{5RC} dt = dV_{out}$$

$$-\frac{1}{RC} \left[\int_{t_1}^{t_2} V_{in} dt + \int_{t_1}^{t_2} V_{o1} dt \right] = \int dV_{out} \quad (2)$$

(1) \rightarrow (2)

$$\therefore V_{out} = \frac{-1}{RC} \left[\int_{t_1}^{t_2} V_{in} dt - \int_{t_1}^{t_2} 2RC \frac{d}{dt}(V_{in}(t)) dt \right]$$

$$V_{out} = \frac{-1}{RC} \int_{t_1}^{t_2} V_{in}(t) dt + 2V_{in}(t)$$

$$V_{out}(t) = 2V_{in}(t) - \frac{1}{RC} \int_{t_1}^{t_2} V_{in}(t) dt$$

5 Sanity Check:

- The output of the derivative opamp was a derivative quantity of $V_{in}(t)$. (1)

- The output of the integration opamp was an integral quantity of $V_{in}(t)$, shifted by the integral of the derivative quantity from (1). This makes sense because the second opamp has input schematic similar to an adder, but it also integrates.


6.

Situation: Find the input output relation for the following circuit. Use ideal opamp model. All diodes are identical.

Goal: To derive an expression relating V_{out} to V_{in} using the ideal opamp model.

Plan: To use the "3-zero" rule along with the diode current equation and Nodal analysis to relate V_{out} to V_{in} .


Solution: Redraw / Label:

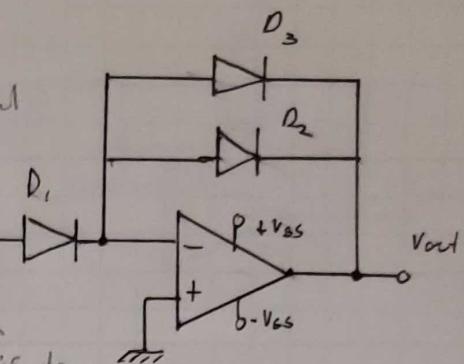

Observe:

$$V_{D1} = V_{in}$$

$$V_{D2} = V_{D3} = -V_{out}$$

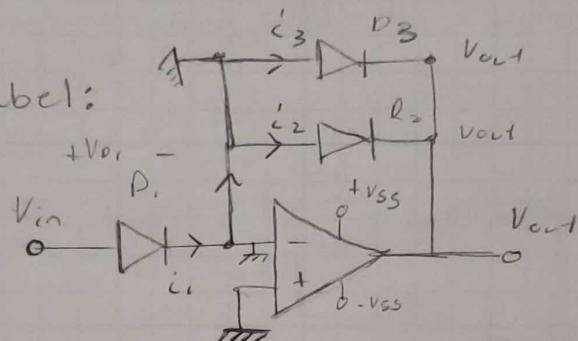

$$\text{Diode Current eqn: } I_d = I_s \exp\left(\frac{V_d}{nV_T}\right)$$

$$V_T = 26 \times 10^{-3} \text{ V}$$

$$\therefore i_1 = I_s \exp\left(\frac{V_{in}}{nV_T}\right)$$

Nodal @ V₋ Node

$$i_1 = i_2 + i_3$$

$$I_s \exp\left(\frac{V_{in}}{nV_T}\right) = 2 I_s \exp\left(-\frac{V_{out}}{nV_T}\right)$$

$$\frac{V_{in}}{nV_T} = -\frac{2 V_{out}}{nV_T}$$

$$V_{in} = -2 V_{out}$$

$$\therefore \boxed{V_{out} = -V_{in}/2}$$

5 Sanity Check:


Here, the diodes can be thought of like resistors assuming forward bias in saturation. Then the effective resistances would be $R_1 = R$, $R_2 = R \parallel R = R/2$, and the inverting amplifier would have a gain: $V_{out} = -\frac{R_2}{R_1} V_{in}$

$$= -\frac{1}{2} V_{in}$$

7


Situation: Find the input-output relation V_{out} vs V_{in} . Use Ideal Opamp Model and $\lambda = 0$ for Mosfet in circuit shown.

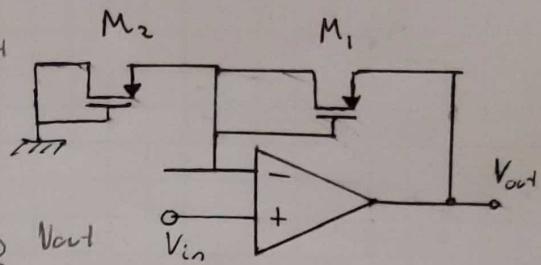Goal: To derive an expression relating V_{out} to V_{in} using $\lambda = 0$ and Ideal Opamp model.



Plan: To use nodal analysis along with the Mosfet current equation to relate V_{out} to V_{in} .

Solution: Redraw / Label:

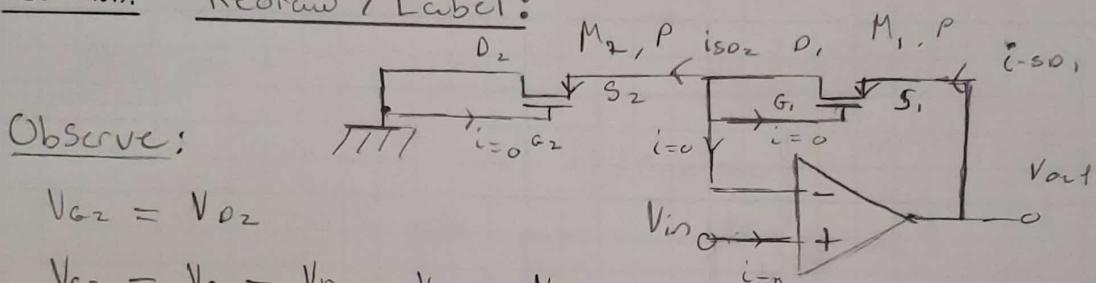

Observe:

$$V_{G2} = V_{D2}$$

$$V_{S2} = V_{G1} = V_{D1} = V_- = V_{in}$$

$$V_{S1} = V_{out}$$

$$\text{MOSFET Current: } I_{SD} = kP_p \left(\frac{w}{L}\right)_p (V_{DD})^2$$

$$\text{where } V_{DD} = (V_{GS} - V_{TH})$$

$$V_{GS1} = V_{in} - V_{out}$$

$$\therefore V_G = V_- = V_+ = V_{in}$$

$$V_{GS2} = V_{G2} - V_{S2}$$

$$= 0 - V_{in}$$

$$\therefore V_{GS2} = -V_{in}$$

$$\therefore I_{DS2} = I_{DS1}$$

$$kP_p \left(\frac{w}{L}\right)_p (V_{DD2})^2 = kP_p \left(\frac{w}{L}\right)_p (V_{DD1})^2$$

$$V_{DD2}^2 = V_{DD1}^2$$

$$V_{DD2} = V_{DD1}$$

$$(-V_{in} - V_{TH}) = (V_{in} - V_{out} - V_{TH})$$

7


(continued)

$$\therefore -V_{in} = V_{in} - V_{out}$$

$$V_{out} = 2V_{in}$$

Sanity Check:Solve using Small Signal instead: $\lambda = 0$

$$M_2 \Rightarrow$$

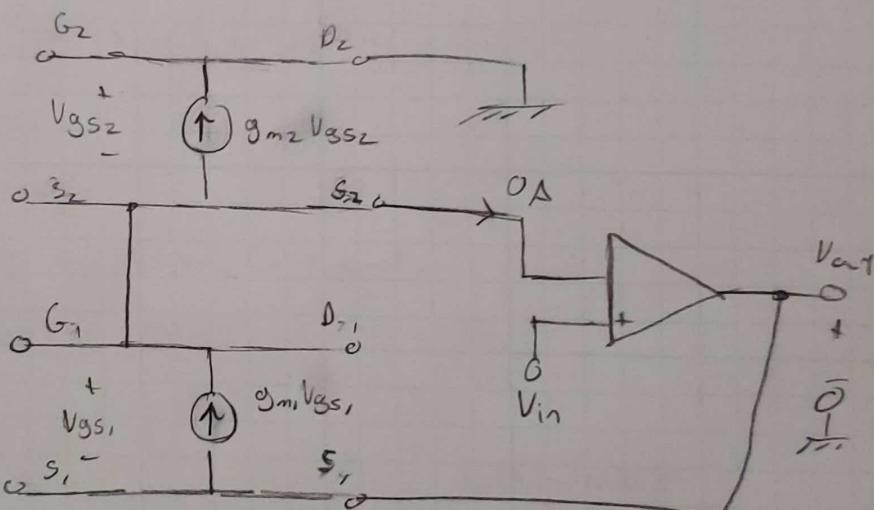

$$M_1 \Rightarrow$$

$$V_{gs2} = -V_{in}$$

$$V_{gs1} = V_{in} - V_{out}$$

KVL: Nodal at S_2 :

$$g_{m2} V_{gs2} = g_{m1} V_{gs1}$$

$$-V_n = V_{in} - V_{out}$$

$$V_{out} = 2V_{in} \quad \checkmark$$

8

1 Situation: Design an OPAMP based circuit that divides two inputs. Derive the circuits input-output relation, i.e.)
 $V_{out} = A(V_{in1}/V_{in2} + B)$

2 Goal: To create an OPAMP circuit to divide two inputs.

3 Plan: To use the equation: $V_1/V_2 = \exp(\ln(V_1) - \ln(V_2))$ as a basis to create a divider opamp circuit using diodes and their associated current equation (exponential).

4 Solution:

$$\begin{aligned} \text{Equation: } V_1/V_2 &= \exp(\ln(V_1) - \ln(V_2)) \\ &= \exp(\ln(V_1) + (-\ln(V_2))) \end{aligned}$$

Needed Topologies:


(2) log opamps

(1) exp OPAMP in Adder Configuration

(1) Inverting BUFFER OpAmp : $R_1 = R_2$

(1) Adder


Block Diagram

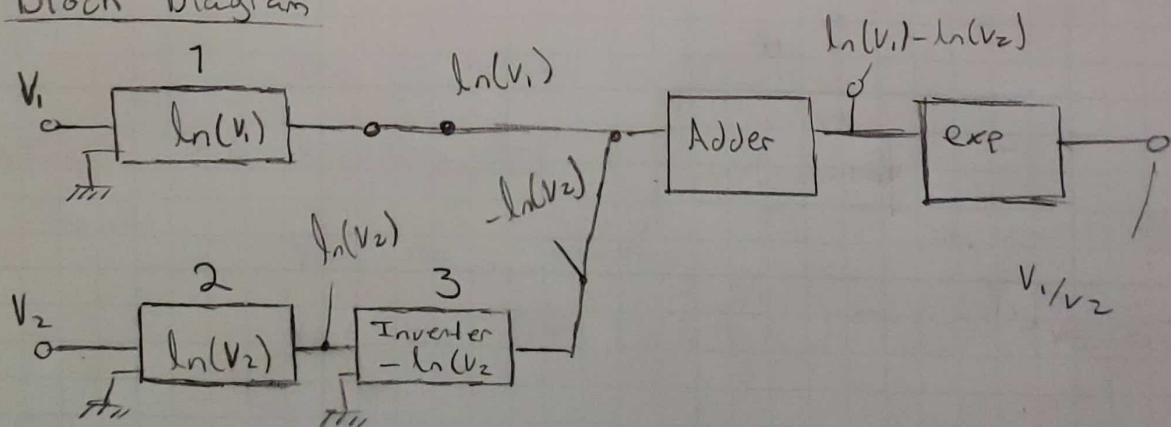

$V_{1/22}$

8

(Continued)

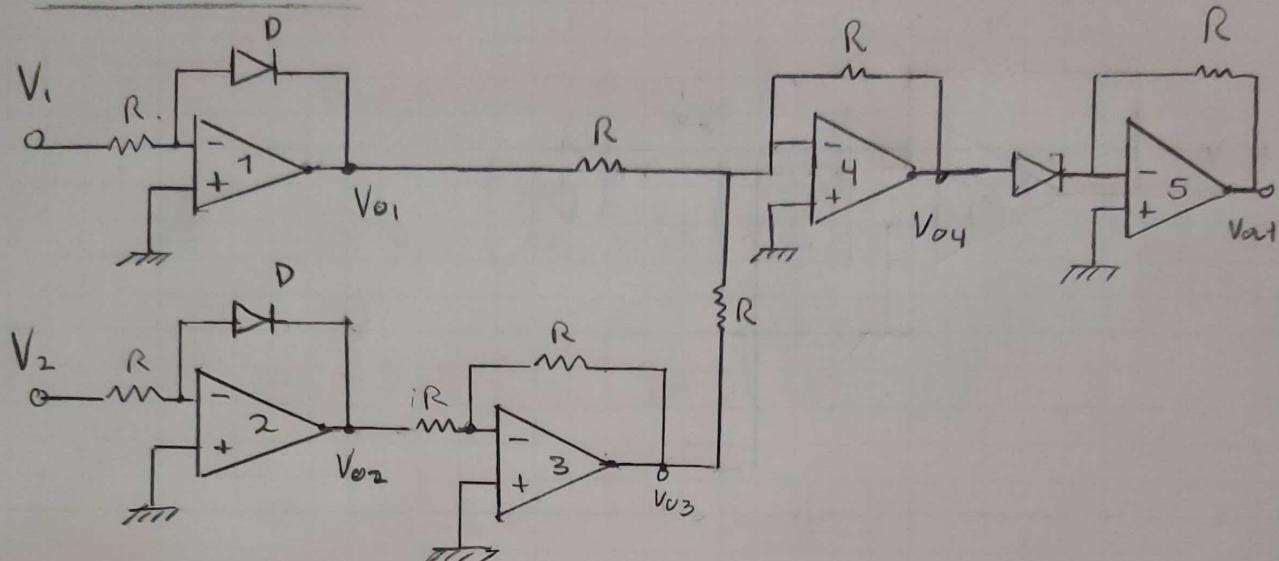Draw SchematicOPAMPS 1, 2: $\ln(V_{in})$

Known:

$$V_{01} = -nV_T \ln\left(\frac{V_1}{I_s R}\right)$$

∴ Lect 38

$$V_{02} = -nV_T \ln\left(\frac{V_2}{I_s R}\right)$$

OPAMP 3: Inverting Amp

Known:

$$V_{03} = -\frac{R}{R} V_{02}$$

$$V_{03} = nV_T \ln\left(\frac{V_2}{I_s R}\right)$$

∴ Known I/O Relation

OPAMP 4: Adder Amp: (with $R_1 = R_2 = R$)

Known:

$$V_{04} = -(V_{01} + V_{03})$$

$$= -(-nV_T \ln\left(\frac{V_1}{I_s R}\right) + nV_T \ln\left(\frac{V_2}{I_s R}\right))$$

$$\therefore V_{04} = nV_T \left(\ln\left(\frac{V_1}{I_s R}\right) - \ln\left(\frac{V_2}{I_s R}\right) \right)$$

8 (continued)

OpAmp 5 : exp

Known: $V_{out} = -I_s R \exp\left(\frac{V_{out}}{nV_T}\right)$

$$= -I_s R \exp\left(\frac{nV_T}{nV_T} \left(\ln\left(\frac{V_1}{I_s R}\right) - \ln\left(\frac{V_2}{I_s R}\right) \right)\right)$$

$$= -I_s R \exp\left(\ln\left(\frac{\frac{V_1}{I_s R}}{\frac{V_2}{I_s R}}\right)\right)$$

$$= -I_s R \exp\left(\ln\left(\frac{V_1}{V_2}\right)\right)$$

$$= -I_s R \cdot \frac{V_1}{V_2}$$


∴ $V_{out} = -I_s R \frac{V_1}{V_2}$

This is in the form $V_{out} = A\left(\frac{V_1}{V_2}\right) + B$

Where $A = -I_s R$, $B = 0$

If a Non-zero B term was desired,
I could put another Adder after
OpAmp 5 with B as another input:

For B

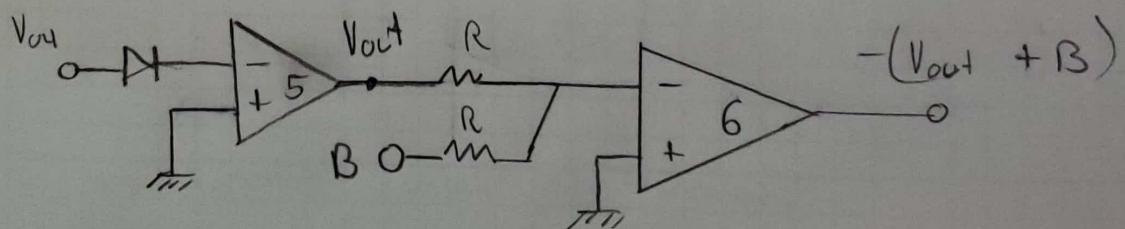

$\frac{V_1}{V_2}$


8 (continued)

Sanity Check:

Check assumptions

OpAmps 1, 2

$$V_o = -V_{out}$$

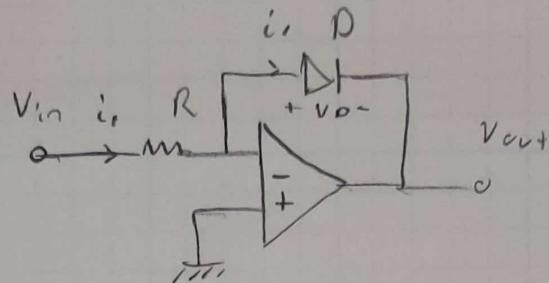

$$i_+ = i_-$$

$$\frac{V_{in}}{R} = I_s \exp\left(\frac{-V_{out}}{nV_T}\right)$$

$$\ln\left(\frac{V_{in}}{I_s R}\right) = \ln\left(\exp\left(\frac{-V_{out}}{nV_T}\right)\right)$$


$$\boxed{-nV_T \ln\left(\frac{V_{in}}{I_s R}\right) = V_{out}} \quad \checkmark$$

OpAmps 3, 4

have been verified in class
multiple times.

OpAmp 5

$$V_o = V_{in}$$

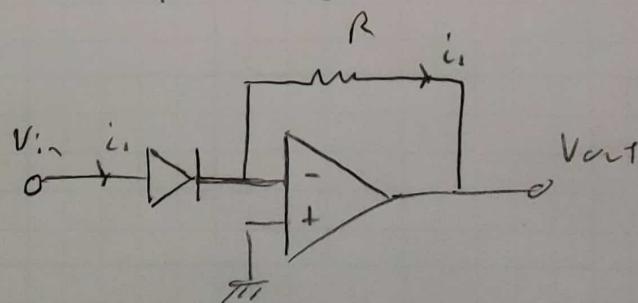

$$i_+ = i_-$$

$$I_s \exp\left(\frac{V_{in}}{nV_T}\right) = -\frac{V_{out}}{R}$$

$$\boxed{V_{out} = R I_s \exp\left(\frac{V_{in}}{nV_T}\right)} \quad \checkmark$$

I am confident with my design.