

Denning

ECE 310 – Microelectronics I

Prof. Suat Ay

Homework #1

Fall 2021


(Due Date: 09/10/2021, 8.30am)

1. (10 pts) Explain what small signal is and AC analysis means to a non-technical person using real life analogies.

2. (30 pts) Find the small signal;


- (10pts) Output impedance (R_{out}),
- (10pts) Transconductance (G_m)
- (10pts) Voltage gain (A_v)

expressions of the following circuit.

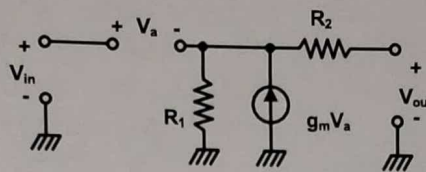


1	10
2	30
3	40
4	20
T	100

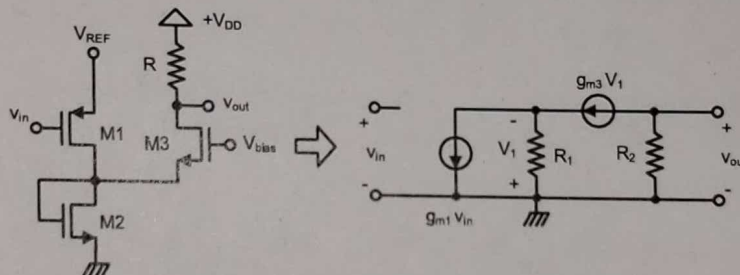3. (40 pts) Analyze following amplifier (small signal equivalent model is shown on the right).



- (10pts) Find small signal input resistance, $R_{IN}=?$
- (10pts) Find small signal output resistance, $R_{OUT}=?$
- (10pts) Find small signal transconductance, $G_m=?$
- (10pts) Find small signal voltage and current gain expression of the amplifier, $A_v=?$ $A_I=?$

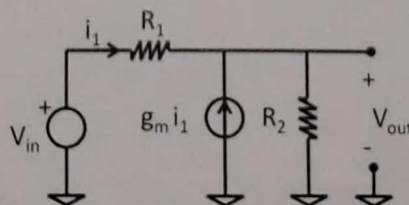4. (20 pts) Find the small signal (a) input impedance ($R_{in}=V_{in}/i_1$) expression and (b) its value for the following circuit. (g_m is a unitless constant)



$R_1=20K, R_2=1K, g_m=50 \text{ mS}$

1.

1 Situation: Explain what Small Signal is and AC analysis means to a non-technical person using real life analogies.

2 Goal To explain the concepts of AC Analysis and Small Signal in Layman's terms.

3 Plan N/A

4 Solution In the field of microelectronics, engineers typically deal with very small voltages. For these voltages to be useful, they usually must be amplified by some means. In most cases, any DC voltage or offset, will have some noise, or unpredictable variation deviating from the offset value. This is called a small signal. We are concerned with small signals because amplifiers will carry them through, resulting in greater distortion of the original signal.

These small signals are created and affected by sound, temperature, light, and other nondeterministic variables.

Small signals are somewhat analogous to standing water. A serene lake that has flat calm water on top would be some DC offset. If someone threw a pebble into the lake, there would be some "small signal" created on the surface. This does not change the depth of the lake - ie the DC offset, but it is a noticeable fluctuation.

AC Analysis aims to measure or quantify how these small signals will affect an output. It can give us models for transconductance and transresistance - or how drastically the small signal will be amplified.


In terms of the lake, amplification factor would tell us how big of waves or ripples would be created by throwing a pebble in.

2(a)

Situation

To derive an expression for the OUTPUT impedance of the given circuit.

Given Circuit:

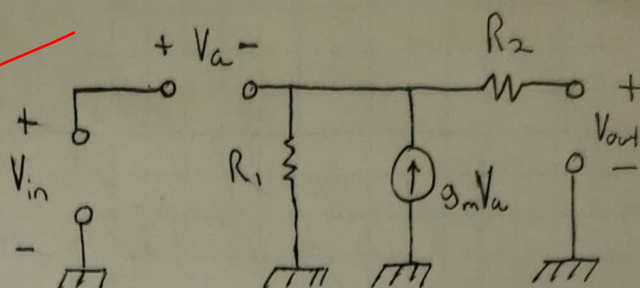


2 Goal To Find a general expression for R_{out}

3 Plan Under the assumption that the given circuit is already the small signal equivalent for some amplifier, Apply a test Voltage V_t between OUTPUT ports and drive V_t/i_t relation, making input source to be zero.

4 Solution

Redraw:

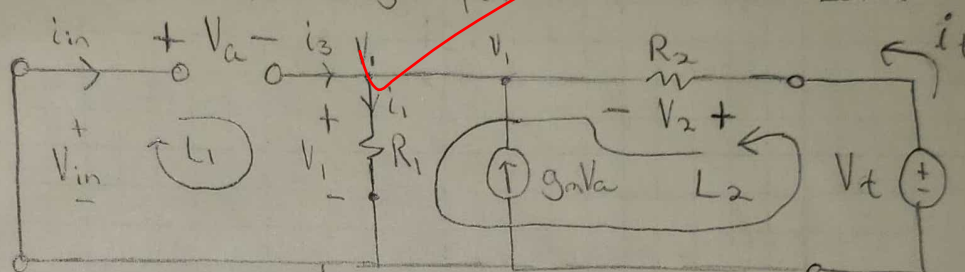

Observe: $R_{out} = V_t / i_t \mid V_{in} = 0$

KCL @ V_1 : $i_t + g_m V_a + i_3 - i_1 = 0$
 $i_t + g_m V_a = i_1$ (1)

* $i_3 = 0$, No current through V_a

KVL on L_1 : $V_{in} - V_a - V_1 = 0$
 $V_1 = -V_a$ (2) * $V_{in} = 0$

Ohm's law R_1 : $V_1 = R_1 i_1$
 $i_1 = V_1 / R_1$ (3)

(3) \rightarrow (1) : $i_t + g_m V_a = V_1 / R_1$
 $i_t = V_1 / R_1 - g_m V_a$ (4)

(2) \rightarrow (4) : $i_t = V_1 / R_1 - g_m (-V_1)$
 $i_t = V_1 / R_1 + V_1 g_m$ (5)

KVL on L_2 : $V_1 = V_t - V_2$ (6)

Ohm's law R_2 : $V_2 = i_t R_2$ (7)

(7) \rightarrow (6) : $V_1 = V_t - V_2$ (8)

Rearrange ⑤ : $i_t = V_t \left(\frac{1}{R_1} + g_m \right)$

⑦ \rightarrow ⑧ : $V_t = V_t - i_t R_2$ ⑨

⑨ \rightarrow ⑤ : $i_t = (V_t - i_t R_2) \left(\frac{1}{R_1} + g_m \right)$

$$i_t = \frac{V_t}{R_1} - \frac{i_t R_2}{R_1} + V_t g_m - i_t R_2 g_m$$

$$i_t + \frac{i_t R_2}{R_1} + i_t R_2 g_m = \frac{V_t}{R_1} + V_t g_m$$

$$i_t \left(\frac{R_2}{R_1} + R_2 g_m + 1 \right) = V_t \left(\frac{1}{R_1} + g_m \right)$$

$$\frac{V_t}{i_t} = \frac{\left(\frac{R_2}{R_1} + R_2 g_m + 1 \right)}{\left(\frac{1}{R_1} + g_m \right)}$$

$$\therefore \frac{V_t}{i_t} = R_{out} = \frac{\left(\frac{R_2}{R_1} + R_2 g_m + 1 \right)}{\left(\frac{1}{R_1} + g_m \right)}$$

5 Sanity Check

$$R_{out} [\Omega] = \frac{\left(\left[\frac{\Omega}{\Omega} \right] + [\Omega] \left[\frac{1}{\Omega} \right] + 1 \right)}{\left(\left[\frac{1}{\Omega} \right] + \left[\frac{1}{\Omega} \right] \right)}$$


$$= \frac{1}{\left[\frac{1}{\Omega} \right]}$$

$$= [\Omega]$$

\therefore My answer is not insane

2(b) Situation

To derive an expression for the TRANSCONDUCTANCE of the given circuit.

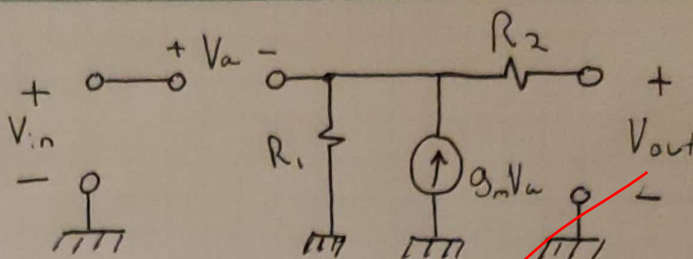2 Goal


To Find a general expression for the circuit's transconductance in terms of R_1 , R_2 and g_m .

3 Plan

To Redraw the circuit Applying a test Voltage V_t between input ports and drive the i_{out}/V_t relationship, where i_{out} is the short circuit output current exiting toward the load. Then solve $G_m = i_{out}/V_t$.

4 Solution

Redraw:

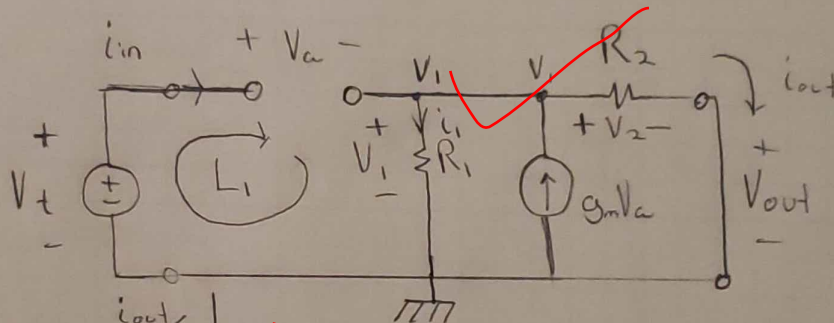

Known: $G_m = i_{out}/V_t$ | $V_{out} = 0$ (shorted)

Observe: $V_1 = V_2$
 $i_{in} = 0$

* V_{out} is shorted, so $V_1 \parallel V_2$
* No current across open Voltage V_a

KCL @ V_1 : $g_m V_a = i_1 + i_{out}$
 $i_{out} = g_m V_a - i_1$ (1)

KVL on L_1 : $V_t - V_a - V_1 = 0$ (2)

Ohm's law R_2 : $V_2 = V_1 = i_{out} R_2$ (3)

Ohm's law R_1 : $V_1 = i_1 R_1$ (4)

(3) = (4) : $i_1 R_1 = i_{out} R_2$
 $i_1 = \frac{i_{out} R_2}{R_1}$ (5)

(5) \rightarrow (1) $i_{out} = g_m V_a - \frac{(i_{out} R_2)}{R_1}$ (6)

2(b) (continued)

Rearrange (2) : $V_a = V_t - V_i$ (7)

(3) \rightarrow (7) : $V_a = V_t - i_{out} R_2$ (8)

(8) \rightarrow (6) : $i_{out} = g_m(V_t - i_{out} R_2) - \left(\frac{i_{out} R_2}{R_1} \right)$ (9)

* Eqn with desired quantities that can be rearranged to $i_{out}/V_t = G_m$

Algebra on (9):

$$i_{out} = g_m V_t - g_m i_{out} R_2 - \frac{(i_{out} R_2)}{R_1}$$

$$g_m V_t = i_{out} \left(1 + g_m R_2 + \frac{R_2}{R_1} \right)$$

$$\frac{i_{out}}{V_t} = \frac{g_m}{\left(1 + g_m R_2 + \frac{R_2}{R_1} \right)}$$

* desired Form
 $G_m = i_{out}/V_t$

$$\therefore \boxed{G_m = \frac{g_m}{\left(1 + g_m R_2 + \frac{R_2}{R_1} \right)}}$$

s Sanity Check

$$G_m = \frac{i_{out}}{V_t} \left[\frac{1}{\Omega} \right]$$

$$= \frac{g_m}{1 + g_m R_2 + \frac{R_2}{R_1}}$$

$$= \left[\frac{1}{\Omega} \right]$$


$$= \frac{\left(\left[\frac{\Omega}{\Omega} \right] + \left[\frac{1}{\Omega} \right] [\Omega] - \left[\frac{\Omega}{\Omega} \right] \right)}{\left(\left[\frac{\Omega}{\Omega} \right] + \left[\frac{1}{\Omega} \right] [\Omega] - \left[\frac{\Omega}{\Omega} \right] \right)}$$

$$= \frac{\left[\frac{1}{\Omega} \right]}{1} = \left[\frac{1}{\Omega} \right] \checkmark$$

* desired
Units For
transconductance \therefore The derived expression for G_m yields the correct unit $[1/\Omega]$

2(c)Situation

To derive an expression for the Voltage Gain, A_v , of the given circuit

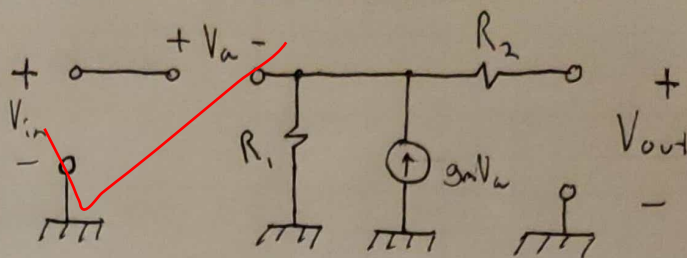Goal

To find a general expression for A_v in terms of R_1 , R_2 , and g_m .

Plan

To Utilize known relationships of Z_{in} , Z_{out} and G_m along with the expressions derived in parts a.) and b.) to create an expression for A_v .

Solution

Known:

$$A_v = \frac{V_{out}}{V_{in}} = \frac{V_{out}}{i_{out}} \times \frac{i_{out}}{V_{in}} = Z_{out} \times G_m$$

$$Z_{out} = R_{out} = \frac{\left(\frac{R_2}{R_1} + R_2 g_m + 1\right)}{\left(\frac{1}{R_1} + g_m\right)}$$

$$G_m = \frac{g_m}{\left(1 + g_m R_2 + \frac{R_2}{R_1}\right)}$$

Substitute:

$$A_v = \frac{g_m}{\left(1 + g_m R_2 + \frac{R_2}{R_1}\right)} \times \frac{\left(1 + g_m R_2 + \frac{R_2}{R_1}\right)}{\left(\frac{1}{R_1} + g_m\right)}$$

$$= \frac{g_m}{\left(\frac{1}{R_1} + g_m\right)}$$


$$\therefore A_v = \frac{g_m}{\left(\frac{1}{R_1} + g_m\right)}$$

Sanity Check

$$A_v [1] = \frac{\left[\frac{1}{\Omega}\right]}{\left[\frac{1}{\Omega}\right] + \left[\frac{1}{\Omega}\right]} = [1] \checkmark$$

\therefore Result is unitless which is desired for gain expression

3(a)

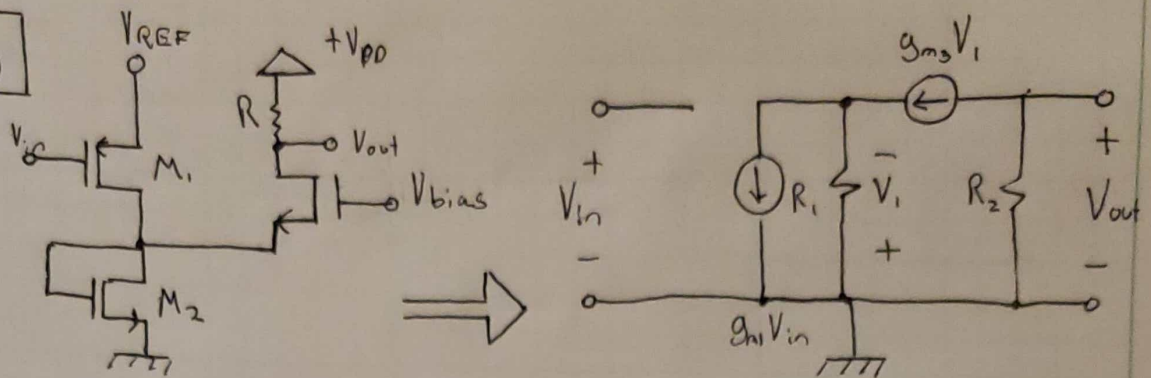1. Situation

To derive an expression for the INPUT resistance, R_{in} , of the Small Signal equivalent of the given Amplifier.

2. Goal

To find a general expression for R_{in} in terms of R_1 , R_2 , g_{m1} and g_{m3} .


3. Plan

To redraw the circuit applying a test Voltage V_t between input ports and drive V_t/i_t relation while leaving the output ports open, (Load disconnected). Then use KVL, KCL, and Ohm's law to derive an expression relating V_t , i_t .

4. Solution

Solve $R_{in} = \frac{V_t}{i_t} \Big|_{R_L = \infty}$ * Load disconnected

Redraw:

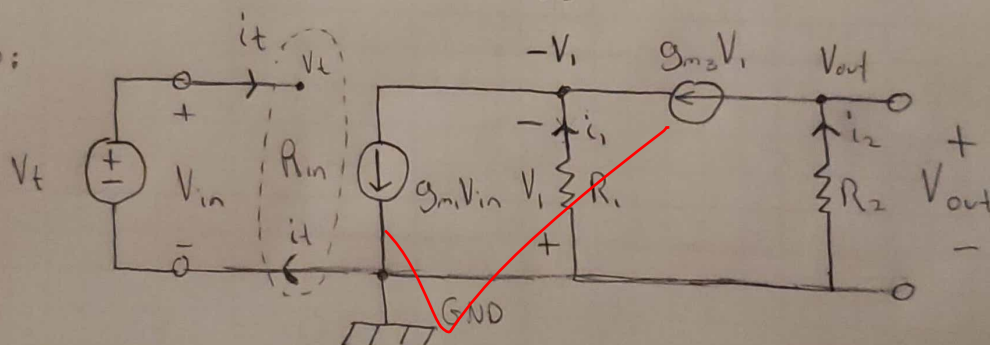

Observations:

$$V_t = V_{in}$$




$$i_t = 0$$

$$\therefore R_{in} = \frac{V_t}{0} = \infty$$

$$R_{in} = \infty$$

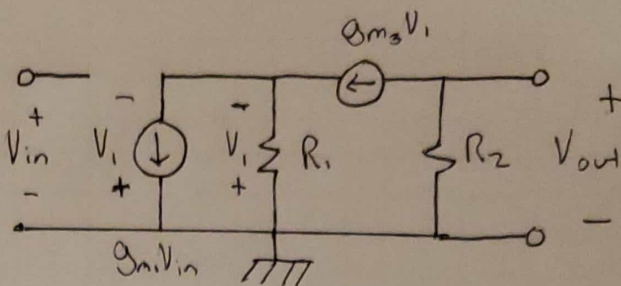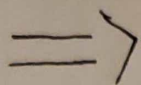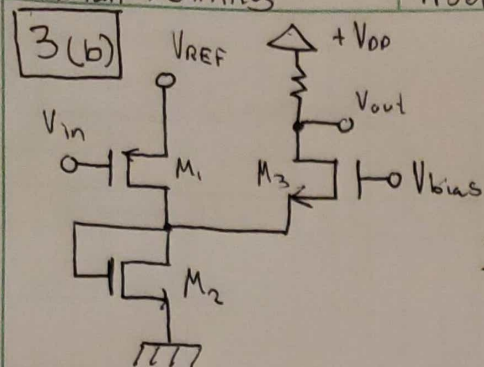5. Sanity Check

$$R_{in} [\Omega] = \frac{V_{in} [V]}{0 [A]} = [\Omega] \checkmark$$



1 Situation

To derive an expression for the output resistance, R_{out} for the given circuit.

2 Goal

To Find a general expression for R_{out} in terms of g_{m1} , g_{m3} , R_1 , and R_2 .


3 Plan

To Redraw the circuit applying a test voltage between Output ports and shorting the input terminals, then use fundamental circuit analysis techniques to find an equation relating V_t and i_t . Solve $R_{out} = V_t / i_t$

4 Solution

$$\text{Solve } R_{out} = \left. \frac{V_t}{i_t} \right|_{R_{in}=0}$$

Redraw:

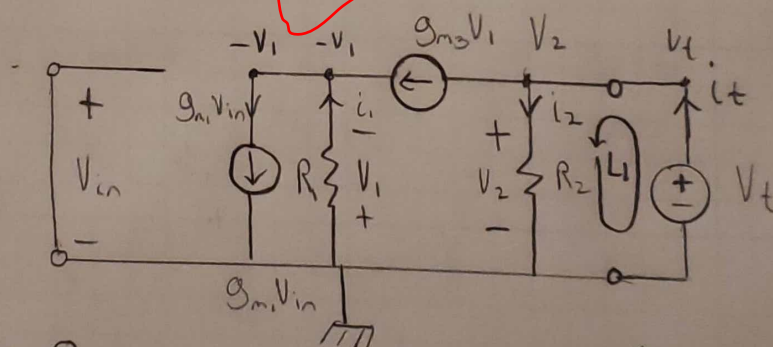

Observe: $V_{in} = 0$

* V_{in} is Shorted

KVL on L_1 : $V_t = V_2$ (1)

Ohm's law R_2 : $V_2 = i_2 R_2$ (2)

KCL @ V_2 : $i_t = i_2 + g_{m3} V_1$ (3)

KCL @ $-V_1$: $g_{m3} V_1 + i_1 = g_{m1} V_{in}$

$-g_{m3} V_1 = i_1$ (4)

* $V_{in} = 0$

Ohm's law R_1 : $V_1 = i_1 R_1$ (5)

(1) \rightarrow (2): $V_t = i_2 R_2$
 $i_2 = \frac{V_t}{R_2}$ (6)

3(b) (Continued)

$$\textcircled{6} \rightarrow \textcircled{3} \quad i_t = \frac{V_t}{R_2} + g_{m3} V_1 \quad \textcircled{10}$$

KCL @ GND : $i_2 = i_1 + i_t + g_{m1} V_{in}$

$$i_2 = i_1 + i_t \quad * V_{in} = 0$$

$$i_1 = i_2 - i_t \quad \textcircled{7}$$

$$\textcircled{6} \rightarrow \textcircled{7} \quad i_1 = \frac{V_t}{R_2} - i_t \quad \textcircled{8}$$

$$\textcircled{8} \rightarrow \textcircled{5} \quad V_1 = \left(\frac{V_t}{R_2} - i_t \right) R_1 \quad \textcircled{9}$$

$$\textcircled{9} \rightarrow \textcircled{10} \quad i_t = \frac{V_t}{R_2} + g_{m3} R_1 \left(\frac{V_t}{R_2} - i_t \right) \quad \textcircled{11}$$

* Rearrange $\textcircled{11}$ to V_t/i_t form to obtain eqn for R_{out}

$$i_t = \frac{V_t}{R_2} + \frac{g_{m3} R_1 V_t}{R_2} - g_{m3} R_1 i_t$$

$$i_t + g_{m3} R_1 i_t = \frac{V_t}{R_2} + \frac{g_{m3} R_1 V_t}{R_2}$$

$$i_t (1 + g_{m3} R_1) = V_t \left(\frac{1}{R_2} + \frac{g_{m3} R_1}{R_2} \right)$$

$$\frac{V_t}{i_t} = \frac{(1 + g_{m3} R_1)}{\left(\frac{1}{R_2} + \frac{g_{m3} R_1}{R_2} \right)}$$

$$\frac{V_t}{i_t} = \frac{(1 + g_{m3} R_1)}{\frac{1}{R_2} (1 + g_{m3} R_1)}$$


$$\frac{V_t}{i_t} = R_2$$

$$\therefore \boxed{R_{out} = R_2}$$

Sanity Check

$$R_{out} [\Omega] = R_2 [\Omega] \quad \checkmark$$

3(c)

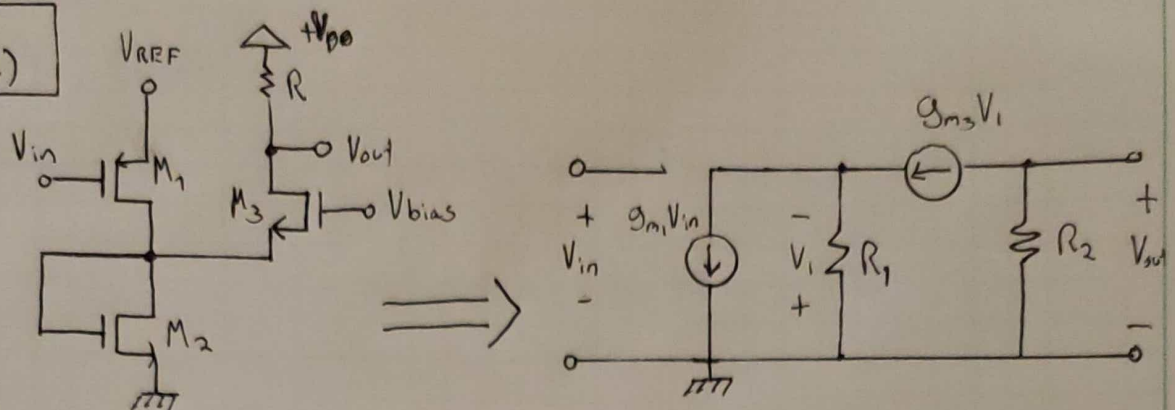


1 Situation To derive an expression for the transconductance, G_m , of the small signal equivalent given.

2 Goal To find a general expression for G_m in terms of R_1 , R_2 , g_{m1} and g_{m3} .

3 Plan To Redraw the circuit applying a test voltage V_t between input ports and short the load. Then use Fund. theorems of circuit analysis to find an equation relating the output current and test voltage. Solve $G_m = i_{out}/V_t$

4 Solution Solve $G_m = i_{out}/V_t |_{z_L = 0}$

Redraw:

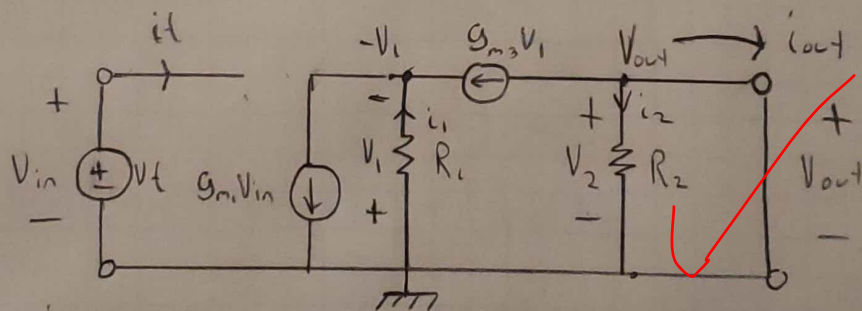

Observe:

$$i_t = 0$$

$$V_2 = V_{out} = 0$$

$$i_2 = 0$$

* Open

* V_{out} Shorted

KCL V_{out} : $i_{out} = -g_{m3}V_1$ (1)

KCL $-V_1$: $i_1 + g_{m3}V_1 = g_{m1}V_{in}$ (2)

Ohm's law R_1 : $V_1 = i_1 R_1$ (3)

KCL @ GND: $g_{m1}V_{in} + i_{out} = i_1$ (4) * $i_t = i_2 = 0$

$g_{m1}V_t + i_{out} = i_1$ * $V_{in} = V_t$

3(c) (Continued)

$$(4) \rightarrow (3) \quad V_i = (g_m V_t + i_{out}) R_i \quad (5)$$

$$(5) \rightarrow (1) \quad i_{out} = -g_{m3} (g_m V_t + i_{out}) R_i \quad (6)$$

* Rearrange eqn (6) to i_{out}/V_t form

$$i_{out} = -g_{m3} g_m V_t R_i - g_{m3} i_{out} R_i$$

$$i_{out} + g_{m3} i_{out} R_i = -g_{m3} g_m R_i V_t$$

$$i_{out} (1 + g_{m3} R_i) = V_t (-g_{m3} g_m R_i)$$

$$\frac{i_{out}}{V_t} = \frac{(-g_{m3} g_m R_i)}{(1 + g_{m3} R_i)}$$

$$\therefore G_m = \frac{(-g_{m3} g_m R_i)}{(1 + g_{m3} R_i)}$$

Sanity Check


$$G_m [v] = \frac{\left[\frac{1}{\Omega}\right] \left[\frac{1}{\Omega}\right] [\Omega]}{[-] + \left[\frac{1}{\Omega}\right] [\Omega]}$$

$$= \frac{\left[\frac{1}{\Omega}\right] [\Omega]}{\left[\frac{\Omega}{\Omega}\right]}$$

$$= \left[\frac{1}{\Omega}\right]$$

$$= [v] \quad \checkmark$$

3(d)

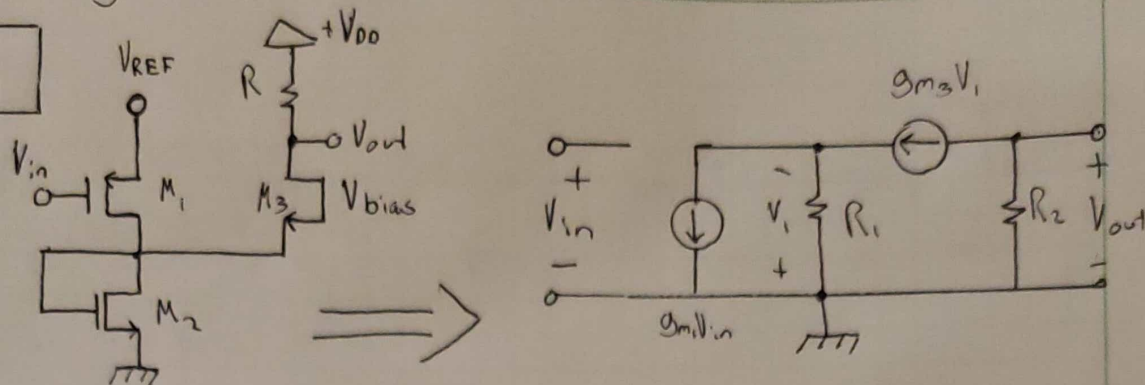1 Situation

To derive an expression for the voltage gain A_v and current gain A_i for the given small signal equivalent.

2 Goal

To find a general expression for A_v and A_i in terms of R_1 , R_2 , g_{m1} and g_{m3} .

3 Plan

To utilize known equations for A_v and A_i in terms of R_{in} , R_{out} and G_m calculated in Parts a, b, and c of this Problem. Plug in derivations from previous parts to known relationships.

4 SolutionKnown:

$$A_v = Z_{out} \times G_m = R_{out} \times G_m \quad (1)$$

$$A_i = Z_{in} \times G_m = R_{in} \times G_m \quad (2)$$

Derived:

$$R_{out} = R_2 \quad * \text{Part (b)} \quad (3)$$

$$R_{in} = \infty \quad * \text{Part (a)} \quad (4)$$

$$G_m = \frac{(-g_{m3}g_{m1}R_1)}{(1 + g_{m3}R_1)} \quad * \text{Part (c)} \quad (5)$$

 A_v : $(3)(5) \rightarrow (1):$

$$A_v = R_2 \left(\frac{-g_{m3}g_{m1}R_1}{1 + g_{m3}R_1} \right)$$

Sanity Check

$$A_v [-] = [\Omega] \left[\frac{1}{\Omega} \right] = [-] \checkmark$$

 A_i : $(4)(5) \rightarrow (2):$

$$A_i = \infty \left(\frac{-g_{m3}g_{m1}R_1}{1 + g_{m3}R_1} \right)$$


$$A_i = \infty$$

Sanity Check:

$$A_i [-] = [\Omega] \left[\frac{1}{\Omega} \right] = [-] \checkmark$$

4 (a)

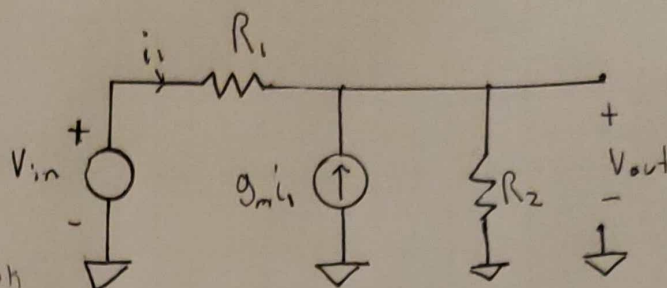1 Situation To derive an expression for the INPUT Resistance R_{in} of the given circuit. (a) then use $R_1 = 20k$, $R_2 = 1k$, $g_m = 50$ to calculate the value of R_{out}




2 Goal To Find a general expression for R_{in} and its value given the specified components above.

3 Plan To Redraw applying a test voltage between input ports and disconnecting the load (open), then use fundamental circuit analysis techniques to find an equation relating the test voltage and test current. Solve $R_{in} = V_t / i_t$ then plug in.

4 Solution

Redraw:

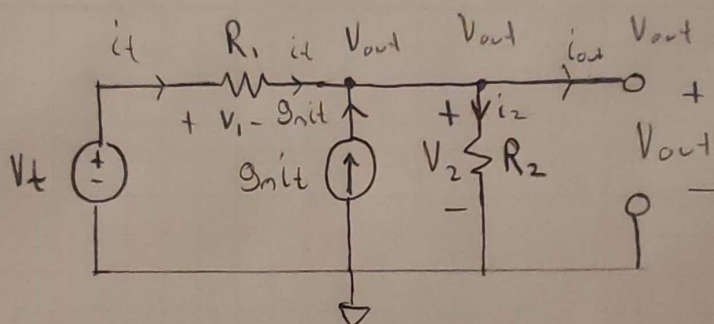

$$R_1 = 20k, R_2 = 1k, g_m = 50$$

Observe: $V_2 = V_{out}$
 $i_{out} = 0$

①

KCL @ V_{out} : $i_2 = i_t + g_m i_t$ ②

Ohm's law R_2 : $V_2 = i_2 R_2$ ③

① \rightarrow ③ $V_{out} = i_2 R_2$
 $i_2 = \frac{V_{out}}{R_2}$ ④

④ \rightarrow ② $\frac{V_{out}}{R_2} = i_t + g_m i_t$ ⑤

KVL Outside loop: $V_t - V_1 - V_{out} = 0$

$$V_t - i_t R_1 - V_{out} = 0 \quad * \quad V_1 = i_t R_1$$

$$V_{out} = V_t - i_t R_1 \quad ⑥$$

4(a) (continued)

$$\textcircled{6} \rightarrow \textcircled{5} \quad \frac{(V_t - iR_1)}{R_2} = i_t + g_m i_t \quad \textcircled{7}$$

Manipulate $\textcircled{7}$ to V_t/i_t form

$$\frac{V_t}{R_2} - \frac{iR_1}{R_2} = i_t + g_m i_t$$

$$V_t \left(\frac{1}{R_2} \right) = i_t \left(\frac{R_1}{R_2} + g_m + 1 \right)$$

$$V_t/i_t = R_1 + g_m R_2 + R_2$$

$$\therefore \boxed{R_{out} = R_1 + g_m R_2 + R_2}$$

Sanity Check

$$R_{out} [\Omega] = [\Omega] + [-][\Omega] + [\Omega] \\ = [\Omega] \quad \checkmark$$

4(b)

Plug in given values to expression derived in (a.)

$$R_2 = 1k, \quad R_1 = 20k, \quad g_m = 50$$

$$R_{out} = 20000 + 50 \times 10^{-3} (1000) + 1000$$

$$\boxed{R_{out} = 21050 \, \Omega}$$

$$71000 \, \Omega$$

Sanity Check

Answer is in Ohms which was the expected result, and is consistent with previous Sanity Check.